
# OPERATING INSTRUCTIONS & SERVICE MANUAL

AM/FM MULTIPLEX STEREO TUNER AMPLIFIER


# SANSUI MODEL 1000 A

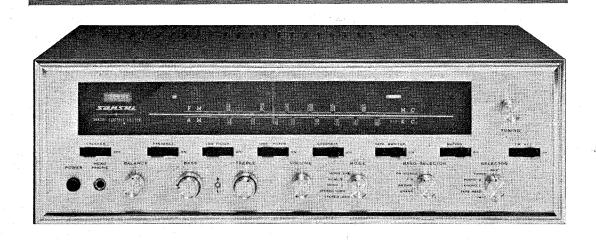


Sansui electric company limited

# SANSUI

# AM/FM MULTIPLEX STEREO TUNER AMPLIFIER

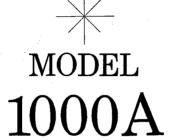

FEATURES	4
SPECIFICATIONS	5
CHARACTERISTICS	5
CONNECTIONS	6, 7
SWITCHES AND KNOBS	8, 9
OPERATIONS	10, 11
GENERAL NOTICE	12, 13
SERVICE NOTE	14, 15, 16, 17
ALIGNMENT	18, 19
PARTS LIST	20, 21, 22, 23
PARTS LAYOUT	24
SCHEMATIC DIAGRAM	25, 26
REMOVALS DISASSEMBLE	27

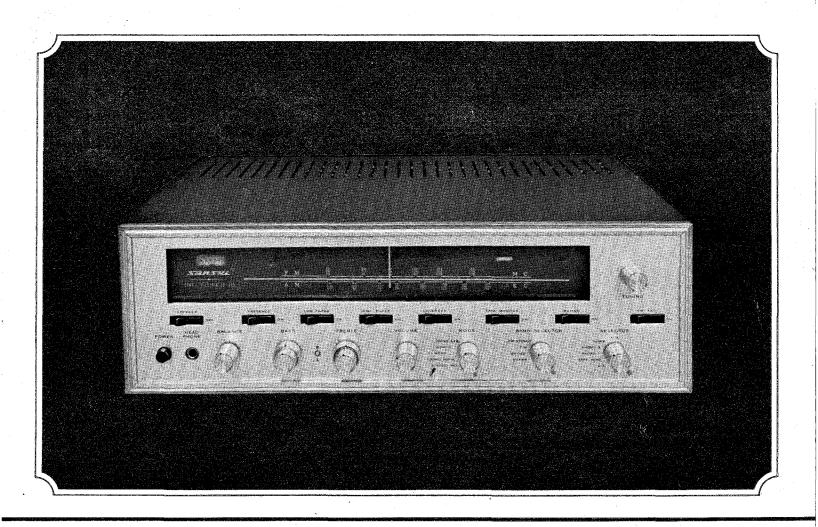

This 1000A has a music power output of 100 watts (50W-50W) and features an amazingly low distortion factor of not more than 0.8% at 76 watts. A high quality amplifier with many exciting features, it is delivered to you with Sansui's fullest confidence.

And this top quality amplifier has a super-sensitive tuner of RF amplifier consisting of two Nuvistors.


Read this instruction carefully before you use the amplifier for the first time.

## **FEATURES**

●New 7591 P.P. produces 80W without distortion (Max. 1% at 1000 cps)

The 7591 power tubes operate in class AB<sub>1</sub>-Push-pull (fixed bias) for high fidelity reproduction. Their combined maximum output is limited to 100 Watts.

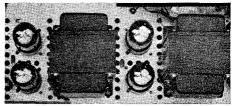Total harmonic distortion at 1 kc is 0.8%,



and even at very low frequency where it is extremely difficult to minimize harmonic distortion, the distortion is limited to not more than 1%. This is quite a feat for a 100 watts amplifier.

Another remarkable feature is the damping factor of 9.5, a figure which is lower than that of triode power tubes coupled in P.P. This is why bass sounds come out with such clarity.

●NFB used in all amplifier circuits, from pre-amplifier to power amplifier

The low distortion of the power amplifier is meaningless if the pre-amplifier generates distortions. This 1000A uses a three-stage amplifier circuit in its intermediate or control amplifier—unlike conventional one-stage control amplifiers—and has all its circuits in a single negative-feedback loop. These make 1000A free from noise and distortion.

●Super-precision transistor pre-amplifier eliminates hum and noise

The exclusive SANSUI four-transistor pre amplifier, which features a transistor circuit factor of 4—as compared with conventional 5~10—and a transistor noise factor of 2 db—as compared with conventional 5 db, eliminates hum and noise, the enemy of high-fidelity reproduction. The amplifier has a



much better S/N ratio and a gain three times larger than vacuumtube amplifier.

◆Highly sensitive two-stage RF amplifier using two Nuvistors and a three-gang variable condenser



The 1000A has an extremely compact high-gain RF amplifier for FM, which uses two cascodecoupled, low noise Nuvistor tubes with a three-gang variable condenser.

Therefore the tuner outperforms conventional single-stage grounded-grid RF amplifiers by 10 db in amplification and assures stable, high-selectivity, high-fidelity reception.

●Double-limiter shuts out noise

The 1000A is equipped with a two-stage noise limiter, which works effectively even where the field intensity is weak. It reliably eliminates a wide variety of noise such as annoying ignition sounds and other interferences.

•Muting switch suppresses noise during channel selection

Unlike conventional FM receivers, which

produce loud noise in the absence of input because their limiters require a certain level of



input voltage to perform their noise-limiting function, the 1000A produces no noise even when not tuned to any station. This is because it has a built-in "Muting switch"

(squelch circuit) which disconnects the audio amplifier stage automatically when tuner input drops below a certain level.

●Three-dimension performance possible with center-channel output terminal

The 1000A has an output terminal for the center-channel amplifier. Connect it to a monaural amplifier, and enjoy a three-dimension effect.





- ●Each channel can be operated independently (Equipped with double-knob control) Each channel has an independent tone control for bass and treble. This makes fine adjustment possible.
- $\ \, \blacksquare \ \,$  Equipped with advanced high-performance accessory circuits

This amplifier is equipped with various advanced accessory circuits such as loudness control, low and high filters, tape monitor, presence, and headphone jack.

Amazing channel separation of 35 db and more ensured by advanced FM multiplex circuit

The adoption of the most advanced switching



matrix method for the multiplex circuit has amazingly improved the performance of the 1000A. The amplifier has a full-fledged AFC, which can be switched off if you like.

### **CHARACTERISTICS**





The AFC enables you to enjoy a stabilized reception of FM broadcast for many hours once you have tuned in.

●Easy-to-see FM multiplex stereo indicator



The FM multiplex stereo indicator actuated helps you tune in FM stereo stations easily and reliably.

Single-stage RF amplifier with threegang variable condenser for AM

The addition of a single-stage RF amplifier to the AM tuner has improved its sensitivity remarkably. This makes it particulary useful for DX reception.

Moreover, it has such an excellent image ratio that no beat is produced between your station and another neighboring station.

Built-in, high-sensitivity ferrite antenna The built-in, high-sensitivity ferrite antenna adds to your listening pleasure by reducing noise to less than that of conventional tu-

#### Features

The input terminals are used for special



connections. When you use a cartridge of less than 2 mv output, employ input transformers (SANSUI'S A-604) and connect to "PHONO-1" terminals on the back of the amplifier.

# TECHNICAL SPECIFICATIONS

### ●AUDIO SECTION

\* Power Output

Music Power: 100 watts total RMS Power Left/Right

40/40 watts (1% harmonic distortion)

\* Harmonic Distortion

1% at 1000 cps and RMS rated power

\* Frequency Response

Over-all:  $20\sim20,000~\rm cps~\pm1~\rm dB$ Power amplifier section:  $10\sim80,000~\rm cps$ 

±1dB
\* Hum and Noise

High level input: 90 dB below rated output
Low level input: 70 dB below rated output
Channel Separation: 55 dB at 1 Kc (PHONO)

\* Input Sensitivity: (for rated output)

Phono 1: 0.5 mV (by using extra matching transformers)

Phono 2: 1.5 mV

Tape Head (NAB): 1.5 mV

Mic: 1.8 mV

Aux 1: 65 mV

Aux 2: 110 mV

Damping Factor: 9.5 at 16 ohms 1000 cps Output Impedance: 8-, 16-ohms

\* Controls and Switches

Bass controls: 26 dB total variation at 50 cps
Treble controls: 21 dB total variation at
10 kc

#### Loudness control

50 cps +7.5 dB, 10,000 cps +7.5 dBVolume control at -30 dB

Low filter: -- 10 dB at 50 cps

High filter: -11 dB at 10,000 cps

Presence switch: 6 dB 50 cps

Mode selector switch

1. Stereo Rev. 2. Stereo Nor. 3. Mono L.

4. Mono R. 5. Mono L+R.

#### Selector switch

1. Mic 2. Tape head 3. Phono 1 4. Phono 2 5. Tuner 6. Aux

\* Other Special Features

Direct tape monitor. Headphone jack.

Center-channel output for connection to a third amplifier. DIN Connector.

### ●FM SECTION

Frequency Range:  $88\sim108\,\mathrm{Mc}$ 

\* Sensitivity

 $1.0\,\mu\mathrm{V}$  for 20 dB quieting at 100% mod.  $1.8\,\mu\mathrm{V}$  (IHFM Standard)

IF-Selectivity: 200 Kc -3 dB

FM Channel Separation: 35 dB at 1000 cps

FM Distortion: less than 1%

FM Stereo Frequency Response

 $50\sim15,000 \text{ cps } \pm 1 \text{ dB}$ 

\* Other Special Features

Muting. Two Nuvistor cascode front end.

Meter tuning. Double limiter. FM stereo indicator

Heavy flywheel tuning. Solid state AFC

### ●AM SECTION

Frequency Range:  $535 \, \mathrm{Kc} \sim 1605 \, \mathrm{Kc}$  IF-Selectivity:  $6 \, \mathrm{Kc}$ .  $12 \, \mathrm{Kc} - 3 \, \mathrm{dB}$  Sensitivity:  $5 \, \mu \mathrm{V}$  (IHFM Standard) IF Frequency  $455 \, \mathrm{Kc}$ 

# ♦TUBES, TRANSISTORS AND DIODES Tubes:

6CW4  $\times$  2(Nuvistor), 6BA6(EF-93)  $\times$  3, 6BE6 (EK-90)  $\times$  1, 6AU6(EF-94)  $\times$  2, 6AQ8(ECC-85)  $\times$  3, 12AX7(ECC-83)  $\times$  2, 12AU7(ECC-82)  $\times$  1, 6BL8  $\times$  1, 6AN8  $\times$  2, 7591  $\times$  4

Transistors:  $2SB-381 \times 4$ 

#### Diodes :

OA-91  $\times$  12, MA-301  $\times$  1, SD-1B  $\times$  2, TC-02P  $\times$  1

#### ●POWER REQUIREMENTS

**Power Voltage:** 100, 117, 240 volts 50, 60 cps

Power Consumption: 180 VA

### **ODIMENSIONS**


Width 17 7/8"

Depth 14 3/16" (Excluding rubber stand)

Height 5 1/2" (Excluding knobs)

●WEIGHT: 44.7 lbs

# CONNECTIONS

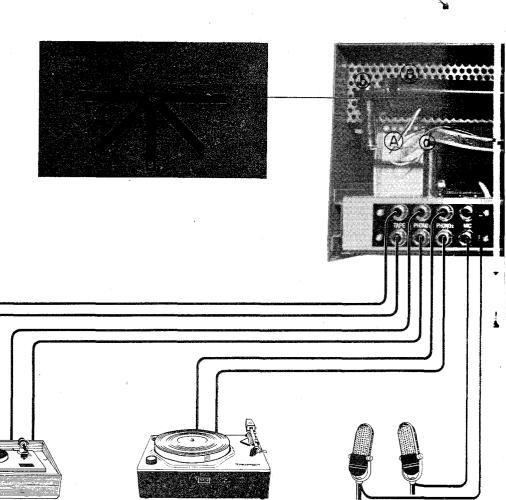

### **ANTENNA**


### Connection of FM antenna

Tape-deck

Connect the attached FM antenna (feeders) to the  $A_1$  and  $A_2$  terminals.

If you live in an area near to broadcasting stations, install the antenna Indoors in "T" shape, choosing its direction so that it brings in broadcasts most effectively. Be careful of the direction and height of the antenna because the input varies considerably.

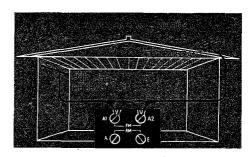When you use this amplifier in a ferro-concrete building or in an area far from the station, the signals become weak and noise stronger. In such a case, use an outdoor antenna exclusively for FM reception. FM sensitivity cannot be increased simply by lengthening the antenna wire. Adjust the height and direction of the antenna while listening to an FM program so that it ensures maximum sensitivity.




### Built-in AM Antenna

less than 2 mV output cartridge player

To receive AM broadcasts, use the built-in ferrite antenna. As shown in the figure, pull the ferrite antenna (B) out of the amplifier by moving angle (A) on axis (a). Move (B) on axis (b) to the point where you can receive the broadcast best. This antenna will perform satisfactrily except in ferro-concrete buildings or in areas remote from broadcasting stations.
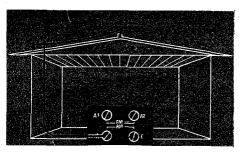
### Connection of AM antenna

When you use the amplifier in a ferro-concrete building or in an area far from the station, the signals become weak and noise stronger. In such a case, use an outdoor antenna built slightly apart from the wall of your house. At the same time, ground the tuner. The direction of the antenna affects tuner sensitivity. Install it so that it can receive broadcasts most effectively. When you use an outdoor antenna, be sure to equip it with a lightning arresting switch to avoid possible danger.



# RECORD PLAYER

Player (magnetic)

Connect the left output of player to the "CHAN-L" on the "PHON-1" or "PHONO-2" input terminals on the back of the amplifier.

Microphone

Connect the right output of player to the "CHAN-R" on the "PHONO-1" or "PHONO-2" on the back of the amplifier.

Connect the power-cord plug receptacle of the player to the power plug on the back of the amplifier.

Either magnetic or crystal cartridge can be used with the 1000A. But, if possible, use the magnetic type for the highest fidelity. When you use the crystal type, connect to the "AUX-1" terminals. When the cartridge output voltage is less than 2 mV, employ input transformers (We recommend Type SANSUI'S A-604) in to the amplifier, and connect to "PHONO-1" terminals on the back of the amplifier. When the cartridge output voltage is over 2 mV, connect to "PHONO-2" terminals on the back of the amplifier.

### \* Note Specifications of


A-604


Frequency Response: 20~20,000 cps (-1 db)
Primary Impedance: 350

Ratio: 1:40 Gain: 32 db Weight: 43 gr

(please contact our sales shop about A-604)

A-6)4 in the amplifier:

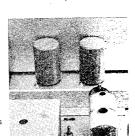

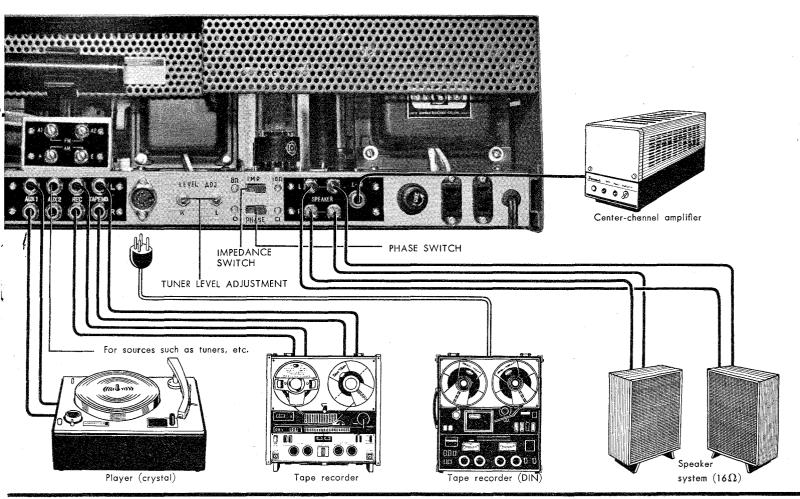

### TAPE RECORDER

This amplifier can be used with a tape recorder for recording and playback and can also play tapes on the tapedeck. If you use a three-head tape recorder which has separate record and playback heads, you can make recordings while listening to a reproduction of the recordings. In other words, this amplifier can be used as a monitor which lets you know the quality of your recordings while they are being made.

### 1. Single-connection tape recorder

A single-connection tape recorder (DIN standard) is to be connected with the single-connection plug to the DIN socket plug on the back of the amplifier.

### 2. Pin-jack tape recorder

- A. Recording: Connect the tape recorder input terminals to L and R (L or R in case of monaural) of the "REC" terminals on the back of the amplifier with shielded wires.
- B. Play back: Connect the tape recorder output terminals ("LINE") to L and R (L or R in case of monaural operation) of the "TAPE MON" terminals on the back of the amplifier.
- 3. Playing tapes on the tape deck

Connect the tape deck output terminals to L and R (L or R in case of monaural operation) of the "TAPE" terminals on the back of the amplifier.

### **MICROPHONE**

You can use a microphone with this 1000A. Any high-impedance (50-kilo-ohm) crystal, dynamic or velocity microphone is acceptable.

Connection: Connect the microphone to L or R of the "MIC" terminals on the back of the amplifier. When you use two microphones, connect one to L and the other to R.

# **SPEAKERS**

### Stereophonic reproduction

Connect the polarity of the left-hand speaker to the upper L terminals of the "Speaker" on the back of the amplifier. Connect (+)'s of the speakers to the (+) terminals. Connect the polarity of the right-hand speaker to the lower R terminals of the "Speaker" on the back of the amplifier. Connect (+)'s of the speakers to the (+)terminals. Switch the impedance switch of the amplifier in accordance with the impedance  $(8\Omega \ \text{or} \ 16\Omega)$  of the speakers.

\* If you find that the sounds from both speakers do not mix well but leave a vacuum of sounds midway between the speakers, you can conclude that the amplifier and the speakers do not match in polarity. In such a case, reverse the phase switch in the opposite direction.

### Monaural reproduction

( 1 ) When you use one speaker system for monaural reproduction, connect the L and R speaker terminals of your amplifier as indicated


in the figure.

- (2) In case an  $8\Omega$  speaker is employed, set the impedance switch at  $16\Omega$ ; in case a  $4\Omega$  speaker is used, set the switch at  $8\Omega$ .
- (3) Be sure to keep the phase switch at "NORMAL (O)".
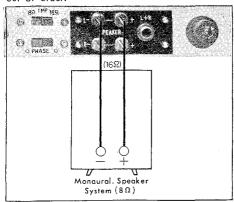
# Three-dimension stereophonic reproduction

This amplifier is equipped with a terminal for a center-channel amplifier so that it can be used for three-dimension reproduction. To do this, refer to the special usage shown on the page 11.

\* When you use two pairs of speakers for stereophonic reproduction, make sure that the speaker output terminal connections do not touch each other and that the terminals are connected properly. If the connections are faulty, your amplifier will not work satisfactorily and may go out of order.



# SWITCHES AND KNOBS



### **OPOWER**

This switch is used for connecting and disconnecting the power supply. Push the button for power. Push it again to shut it off. The switch also activates and deactivates the power supply plug receptacles on the back of the amplifier.

### **@HEADPHONE JAOK**

When you want to avoid disturbing others or when you use the amplifier as a monitor, connect the headphones to this jack. You can still enjoy stereophonic reproduction through the headphones. For this purpose, you can use any kind of headphones or earphones if their pulgs fit into the jack. But use dynamic headphones designed for stereophonic reproduction, if possible.

### **3**BALANCE

This knob is used to adjust the balance of volume between the right and left speakers for the best stereophonic effect. Make an adjustment while listening to the sounds of both speakers. When the amplifier is adjusted properly, you feel as if the sound comes from a point midway between the two speakers (in monophonic reproduction).

### 

These control the tone of L and R speakers and each channel's bass and treble can be operated independently. Turn it clockwise for louder reproduction and to reduce turn counterclockwise. The knobs out-side are the controls for the right side speakers and inside-knobs are the controls for the left side speakers.

### @VOLUME

Output power from the amplifier is adjusted with this control.

Do not fast turn this volume knob, or it may break small power capacity speakers.

### **⑦MODE**

STEREO REV: Reverses the sounds from speakers. Signals from Channels L and R are reproduced from the speaker R and L respectively.

STEREO NORM: Signals from L and R are reproduced by L and R speakers respectively. Maximum (peak) power output is 50 Watts per channel, 100 Watts total.

MONO. L: Signals from L is reproduced by L and R speakers at the same time. (R input not operative) Maximum output is 100 Watts.

MONO R: Signals from R is reproduced by L and R speakers at the same time. (L input not operative) Maximum output is 100 Watts.

 $\label{eq:monosity} \begin{tabular}{lll} MONO L+R: & Mixed L and R sounds from \\ & both speakers. \end{tabular}$ 

STEREO	(A) CHAN-L	CHAN L A
NOR.	B CHAN R	— CHAN R — 3 →
STEREO	A)— CHAN-L >	CHAN B +
REV	B-CHAN-R	CHAN-R — A
MONO-	(A) CHAN L	CHAN-L A
L	CHAN-R	CHAN-R A
MONO-	CHAN-L	CHAN-L -<9- +
R	B CHAN R	CHAN R - 10
MONO-	A CHAN-L	r CHAN-L
L ∓ R →	(B)— CHAN-R	CHAN R — <ab td="" →<=""></ab>

### **®BAND SELECTOR**

SHARP: Set the control to sharp when selectivity is preferred in listening to AM.

BROAD: When total quality is preferred in listening to AM Broadcast.

FM: For Listening to FM Broadcast.

FM STEREO: When Listening to FM Stereo broadcast.

If FM stations are near to you, listen to monaural FM broadcasts at this position. When FM stereo starts, you can enjoy it without any further functioning of the switches, provided that the MODE switch is in STEREO position.

### SELECTOR

MIC: For microphone.

TAPE HEAD: For input from tape deck.

PHOMO-1: For a turntable equipped with a cartridge of little output, less than 2 mV. For its operation, Matching Transformers (Sansui's A-604 recommended) are required to be employed.

PHONO-2: For a turntable equipped with a standard cartridge of 2 mV.

TUNER: For AM, FM radio reception.
AUX: For input from external circuit.

#### **@SPEAKER**

When listening with headphones, speaker sound is eliminated by setting the speaker switch to the off position.



### **MPRESENCE**

If the tone control alone is used for base compensation, slightly higher frequencies are compensated at the same time. To avoid this, turn this switch "ON".

This sets the turnover at 160 cps, changing speaker damping and frequency response characteristics to compensate base. As a result, all sounds become impressive and you can enjoy clear, magnificent base.

### **12LOW FILTER**

For eliminating very low frequency noises, such as those produced by a phono turntable or a tape deck.

### **13 HIGH FILTER**

For eliminating annoying noises produced by record scratch, radio "static", whistles and other interferences.

### **@LOUDNESS**

When sound volume is at a low level, you feel as if bass and treble are missing. In such a case, turn this switch "ON" to compensate bass and treble. This will make you feel as if you were present at an actual concert.

### **®TAPE MONITOR**

When switched on, sound being recorded through a three-head tape recorder can be played back through the amplifier. This switch should be on only when playing back from a tape recorder. While the tape is being recorded, it is possible

to listen to the program and monitor the recording at the same time.

When not recording, set to off.

### **6 MUTING**

Turn this switch on to eliminate the noise you hear when not tuned to any station. Keep it on while tuning. However, if the muting switch is kept on when you receive weak signals, the sound may be distorted or reception may become impossible. In such a case, switch off the muting circuit.

### **@FM-AFC**

This prevents FM signals from drifting. This is likely to happen because of the very high frequencies used. If it occurs, the tonal quality deteriorates or you cannot hear the program at all. To avoid this, switch on the FM-AFC after tuning in the station of your choice. If you switch on the FM-AFC before tuning, you may not be able to tune the tuner accurately. If the FM-AFC is kept on even when there are a number of stations nearly, you may suffer from their interference. In such a case, switch off the FM-AFC.

### **18 TUNING INDICATOR**

When tuning in the FM or AM station of your choice, set the dial pointer to the position where you can get a maximum indication on the tuing

## MULTIPLEX STEREO INDICA-

#### TOR

When the tuner receives signals from an FM station broadcasting multiplex, this indicator lights up to show that it is receiving a stereo broadcast. The indicator never lights when the tuner is receiving a monaural FM broadcast. It lights up when the tuner is switched on, but goes off before long.

# 20 STEREO & MONO INDICATOR Indicates Stereo and Mono reception.

### 20 DIAL SCALE

### **22 TUNING**

For tuning FM and AM broadcasts, rotate the tuning knob to select desired station on FM or AM dial scale while ovserving the tuning indicator for the point of best reception.

# RECORD PLAYER OPERATION

- 1. Set the "SELECTOR" switch at "PHONO-1" or "PHONO-2".
- 2. Set the "MODE" switch at "STEREO-NORM" or "STEREO-REV" (at L or R in case of monaural operation).
- 3. Switch on the player, put on a record and adjust the number of revolutions as neccessary before placing the pickup on the record.
- 4. Balance the sound from both speakers by means of the "BALANCE" knob.
- Adjust the amount of sound by means of the "VOLUME" knob. Other adjusting knobs and switches can be used to get the most satisfactory repoduction.
- \* When you play a monaural record on a stereo record player, follow the same procedure as for stereo records. This will give you better results. \* If you feel that left and right are reversed when playing a stereo record, turn the "MODE" switch to "STEREO-REV".
- \* To balance the sounds from both speakers, play a monaural record in the same way as a stereo record and adjust the "BALANCE" knob in such a way that you feel the sound comes from a point midway between the right and left speakers.

# TAPE RECORDER OPERATION

### Recording

- 1. Set the "SELECTOR" switch at the proper position according to the program source (broadcast or record) you are going to record.
- 2. Set the "MODE" switch at "STEREO-NORM" or "STEREO-REV" (for stereophonic recording). "MONO-L" or "MONO-R" (for monaural recording), or at MONO-L+R. (for monaural recording of a stereophonic source).
- 3. Prepare a tape recorder for recording.
- 4. Operate the recorder and amplifier adjusting knobs and switches properly.

### Playback

- 1. a. Tape deck
- Set the "SELECTOR" switch at "TAPE".
  - b. Tape recorder
- Set the "TAPE MON" switch at "ON".
- 2. Set the "MODE" switch at "STEREO-NORM" or "REV" (for stereo), at "MONO-L" or "R" (for monaural), or at MONO-L+R (for double track monaural).
- 3. Set the tape recorder in the Play position.
- 4. Other adjusting knobs and switches should be set for the most satisfactory reproduction.

### Tape Monitoring

To use your amplifier as a monitor for a threehead tape recorder, follow the same procedure as the one for playing tapes on a recorder.

When you use a recorder, read the instruction manual carefully to avoid error in connection and operation. Unless you use your amplifier with a tape recorder, be sure to switch off the "TAPE MON" switch.

Connecting tape recorder can be done using either a single connection plug or by pinjacks. The single-connection plug conforms with German DIN

standard specifications. It makes it easier to connect the tape recorder to the amplifier because it has a five-pin plug for both record and playback.


# MICROPHONE OPERATION

- 1. Set the "SELECTOR" switch at "MIC".
- 2. Set the "MODE" switch at "STEREO-NORM" or "STEREO-REV" (when you use only one microphone for stereophonic effect).
- At "MONO-L" or "MONO-R" (When you use only one microphone for monaural reproduction), or at MONO-L+R (when you use mixing two different program sources from two microphones).

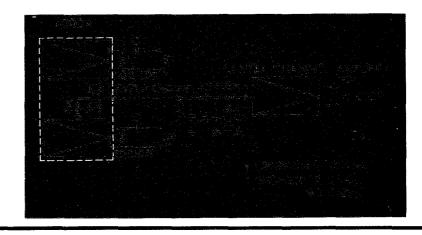  3. Other adjusting knobs and switches can be

used for the most satisfactory reproduction.

This amplifier accepts only high-impedance microphones. You cannot get the best performance if you use too long microphone cord, which causes various problems and reduces treble. This amplifier has separate tone controls for right and left speakers. You will find this feature very useful when you use one microphone for music and another for voice. Further, it gives added varsatility to the amplifier, particularly when you record on a tape what is picked up by microphones,



## **BROADCASTING RECEPTION**

### A. FM broadcast reception

- 1. Set the "SELECTOR" switch at "TUNER" (lamp lights on tuning meter),  $% \left( \frac{1}{2}\right) =\frac{1}{2}\left( \frac{1}{2}\right) \left( \frac{1}{2}\right)$
- 2. Set the "BAND SELECTOR" switch at "FM".
- 3. You can receive at any point of the "MODE" switch.
- 4. FM-AFC switch at OFF.
- 5. Tune in the station of your choice by means of "TUNING" knob using the dial and the Tuning Meter.
- 6. Set the "MUTING", if noise comes out during channel selection.
- 7. When you have finished channel selection, switch on the "FM-AFC".
- 8. Use other switches and knobs according to your needs.

### B. AM broadcast reception

- 1. Set the "SELECTOR" switch at "TUNER".
- 2. Set the "BAND-SELECTOR" switch at "SHARP".
- 3. You can receive at any point of the "MODE" switch.
- 4. Tune in the station of your choice by means of "TUNING" knob using the dial and the Tuning Meter.
- 5. Set the "BAND SELECTOR" switch at "BROAD" after the selection of a channel when you want to hear real Hi-Fi sounds.
- 6. Use other switches and knobs according to your needs.

### C. FM MPX stereo reception

- I. Set the "SELECTOR" switch at "TUNER".
- 2. Set the "BAND-SELECTOR" switch at "FM-MPX".
- 3. Set the "MODE" switch at "STEREO-NORM" or "STEREO-REV".
- 4. Tune in the station of your choice by means of the "TUNING" knob using the dial and the Tuning Meter.

The moment tuned in a FM stereo station, the FM Stereo Indicator lights up. It lights up immediately after the tuner has been switched on, but goes off soon.

- 5. The "TUNING" and "FM-AFC" switches are operated same with the FM broadcast reception.
- 6. Control the balance of the left and right speakers with the "BALANCE" knob.
- 7. Use other switches and knobs according to your needs.

### FM broadcast

FM broadcasts are characterized by excellent tonal quality and freedom from noise. These features are used for compatible multiplex broadcasts. But sometimes we have to prevent the signals from FM station from drifting. This is likely to happen because of the very high frequencies used. If this occurs, the tonal quality deteriorates or you cannot hear the program at all. To avoid this, switch on the FM-AFC after tuning in the station of your choice.

### FM stereo broadcast

The FM stereo broadcast has two kinds of systems for the reception. One is FCC method, and the other CROSBY (FM-FM) method. This amplifier uses the FCC method. The FCC method comprises the sum of signals from the right and left and the difference between the two. The latter serves as the code for the stereophonic effect. When signals are weak and noise is strong during stereophonic reception, the built-in noise filter or high filter is used to eliminate the high frequency noises.

### AM broadcast

Set control to "SHARP" when selectivity is preferred in listening to AM broadcast. It is recommended to select the program at this position first, and then set to "BROAD". When tonal quality is preferred, set control to "BROAD". In the areas far from stations or noises and mixed signals alive, you better turn to "SHARP" for the best reception.

## SPECIAL OPERATION

### ●THREE-DIMENSIONAL STEREO

This 1000A amplifier has an output terminal for the center-channel amplifier.

The center-channel mixes the left and right sounds to produce the three-dimensional effect.

To do this, connect the input terminal of the center-channel amplifier (monaural amplifier) to the center-channel output terminal of 1000A at the right of the speaker terminal board with shielded

Connections are as the above figure.

## **GENERAL NOTICE**

### HOW TO ELIMINATE NOISE

#### ●AM Broadcast Reception

Noise during AM broadcast reception can often be eliminated just by changing the position of the antenna.

In an area far from the station or in the mountains where radio waves cannot reach easily, or in a ferro-concrete building or a block of such buildings, the waves are not received well, resulting in unstable reception and much noise. In such a case, connect a vinyl covered wire provided to the AM antenna terminal and stretch it along a pillar, lintel or ceiling in such a way that the signals come in best. If this does not reduce noise or improve sensitivity, erect an antenna outside the building, slightly apart from the wall.

In addition, some noises are peculiar to a certain broadcasting frequency. These result from the nature of AM waves. In some cases, they can be eliminated by grounding the amplifier or reversing the power cord plug-receptacle connections.

### ●FM Broadcast Reception

Noise during FM broadcast reception can be generally attributed to either of these: insufficient antenna input or interference from other electrical appliances.

Antenna input is insufficient when the antenna is not installed properly or when the station is far away. Extend and fix the attached antenna in such a position that noise is minimized.

If this does not prove effective, erect an outdoor antenna exclusively for FM reception in such a position that you can receive the broadcast most effectively.

To prevent noise, avoid using an unneccessary long antenna wire.

FM reception is affected considerably by the conditions of transmission by stations: power and antenna efficiency. As a result, you may receive

one station quite well while having difficulty in receiving another station.

#### ●Common to AM and FM

In an area occupied by many ferro-concrete buildings, you may notice noise which occurs at a particular time of day. This type of noise can be easily distinguished from those described above. To eliminate such noise, attach a noise arrester to the electrical appliances or to the power source of your amplifier.

#### Monophonic Reception of FM Multiplex Stereo Broadcasts

When you tune to an FM multiplex program, you may notice a noise which does not accompany monaural FM broadcasts. This does not mean that your tuner is out of order. In such a case, turn on the noise filter. In some cases, you can eliminate the noise by setting the treble knob of the amplifier flat or lower.

When you receive FM multiplex stereo broadcasts monophonically—with the selector at "FM"—the sounds from both speakers mix into a monaural reproduction as if you tune to an ordinary monaural FM station. Use this method if you find too much noise when receiving an FM multiplex stereo broadcast because the waves, field intensity or input is inadequate.

### GROUNDING THE AMPLIFIER

Noise can sometimes be reduced by grounding the amplifier. To do this, connect the "E" terminal on the antenna terminal board on the back of your amplifier to a copper rod or plate buried deep in the ground. Use a vinyl covered or enamelled wire to make the connections.

### CONNECTIONS

When you connect your amplifier to a tape recorder or tuner, be sure to use an adequately

thick shielded wire. If you use an untwisted vinyl covered wire like those used for the lights, you will suffer from hum. Furthermore, do not use a wire longert han 2 meters (about 6.5 ft.), because the longer the connecting wire is, the greater the attenuation of treble becomes. For connection to a tuner or FM adaptor, use a wire 1 to 1.5 meters (about 3.3 to 4.8 ft) long. When you use the amplifier for monaural reproduction, it is easier for operation to use the upper R terminal for connection. Be sure to set the "MODE" switch to the connected channel.


### HUM AND HOWLING

When you play a record or tape, you may sometimes hear unpleasant humming or howling. This does not mean that your amplifier is defective. In most cases, humming or howling is a result of these causes:

If you place a record player on or near the speaker box, the vibrations of the speaker cabinet caused by the sound waves from the speaker are transmitted to the player and cause howling. To prevent this, keep the record player away from the speaker cabinet or put a thick cushion between the player and the cabinet.

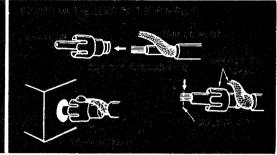Low, buzzing sound will also be produced if you do not use shielded wire for connection. If this is not the case, examine the connections closely. Make sure that the earth and live end are not reversed so that the motor and arm are inadequately grounded.





### SPEAKER POLARITY

If the phase (polarity, viz. + and -) of the right and left speakers is reversed, the sounds at the center over the frequency range become weak. You will particularly sense an attenuation of bass. To make sure that speaker palarity is all right, play a monaural record on a stereo record player. If the polarity is reversed, you will have the result mentioned above. In such a case, reverse the polarity switch in the opposite position. When both speakers are thus made to agree in polarity, you will feel as if the sound is coming from a single speaker placed just between the right and left speakers.

### **FUSE**

The amplifier does not work when the fuse is blown. In such a case, disconnect the power cord and replace the fuse on the back of the amplifier. Use a 4-ampere fuse enclosed in a glass tube. Never risk the danger of using fine wire or a fuse of a larger capacity as a substitute. If the fuse has burnt out because the amplifier is out of order, locate the trouble and repair it before replacing the fuse. The fuse blows if you use an AC plug receptacle larger shan the specified capacity (30 VA).

### HEAT GENERATED BY AMPLIFIER

The top of the amplifier cover becomes considerably hot after many hours of continuous operation. But this should not worry you because air vents are provided on the top and back of the cover. If you place something on the amplifier or put the amplifier in a closed box, or keep its front panel facing up, it might damage your amplifier.

When you mount this amplifier in a cabinet, it is better to take off the top cover and use a cooling fan.  $\label{eq:coverage} \widehat{\text{a}}$ 

### CONNECT LEADWIRES PROPERLY

Connect leadwires properly to the speaker and other input and output terminals. If connections are loose or touch other parts, your amplifier will not work properly. Moreover, it may produce noise. If you use your amplifier in such a way for a long time, it may eventually break down. Finally, read the instructions for your tuner or tape recorder carefully before you connect it to your amplifier.

### AC PLUG RECEPTACLES

Of the two AC plug receptacles provided on the back of the amplifier, the one nearer to the output terminals can be switched on and off by means of the power switch, while the other one cannot. These receptacles have capacities of 30 VA and 120 VA, respectively. If appliances requiring more than 150 VA are connected to these receptacles, the amplifier fuse will blow off or cause other trouble. Be sure not to overload these receptacles.



# SERVICE NOTE

	Symptoms (1)	Symptoms (2)	Likely defective places
When the Power switch is pushed, electric sup- ply is not on.	A. Poor power switch. B. Poor power cord. C. Poor plug contact. D. Blown fuse.	(In case the fuse blows again upon fitting a new one)	Replace it. Replace it. Replace it. Replace the plug or make the plug contact better. Replace it. Short-circuit rearing in the power transformer $(T_{10})$ or short-circuit of path condenser $(C_{149})$
When the power switch is pushed, electric supply is on.	A. The amplifier does not work at all.	Broken wires of vacuum tube heaters.     In case there is something wrong in the vacuum tube and voltage in resp. places     In case there is nothing wrong in the vacuum tube and voltage in resp. places	$V_1 \sim V_{21}$ and silicon diodes. Check the places where there is something wrong in voltage. Check the input circuit after AUX.
	B. Only the FM tuner does not work at all.	<ol> <li>Broken wires of vacuum tube heaters in the FM system.</li> <li>In case there is something wrong in the vacuum tube and voltage in resp. places in the FM system.</li> <li>In case there is nothing wrong in resp. places in the FM system.</li> </ol>	V <sub>1</sub> ~V <sub>7</sub> , V <sub>10</sub> Check the places where there is something wrong in voltage.  Insufficient capacity of C <sub>42</sub> , C <sub>43</sub> . Poor IFT (T <sub>1</sub> ~T <sub>5</sub> ). Short-circuit of C <sub>25</sub> , C <sub>26</sub> , C <sub>27</sub> , C <sub>44</sub> . Trouble in the local oscillating circuit of V <sub>3b</sub> (6AQ8)
	C. Only the FM-MPX system does not work.	<ol> <li>Broken wires of vacuum tube heaters in the multiplex system.</li> <li>In case there is something wrong in the vacuum tube and voltage in resp. places in the multiplex system.</li> <li>In case there is nothing wrong in the vacuum tube and voltage in the multiplex system.</li> </ol>	If the FM tuner works normally, check $V_{11} \sim V_{13}$ . Check the places where there is something wrong in voltage.  If the FM tuner works normally, it is caused by insufficient capacity of $C_{45}$ , $C_{62}$ , $C_{64}$ , $C_{66}$ , $C_{67}$ , and poor $L_{10}$ , $L_{12}$ , $L_{13}$ .
	D. Only the AM tuner does not work	<ol> <li>Broken wires of vacuum tube heaters in the AM tuner system.</li> <li>In case there is something wrong in the vacuum tube and voltage in resp. places in the AM tuner system.</li> <li>In case there is nothing wrong in the vacuum tube and voltage in resp. places in the AM tuner system.</li> </ol>	V <sub>8</sub> , V <sub>9</sub> , V <sub>5</sub> Check the places where there is something wrong in voltage.  Poor IFT (T <sub>6</sub> , T <sub>7</sub> ) and RF coil (L <sub>8</sub> ). Poor diode (OA-91). Short-circuit of C <sub>18</sub> and C <sub>20</sub> . Insufficient capacity of C <sub>39</sub> .
	E. The phono, tape head and mike systems do not work.	<ol> <li>In case of poor TR head.</li> <li>In case of poor contact of the selector switch.</li> <li>In case there is something wrong in the input circuit.</li> <li>Poor condition of the attached appliances connected.</li> <li>Poor coupling condenser 0.05 μF.</li> </ol>	Replace the TR head amplifier unit. Replace it or repair the contact $(S_{1a \cdot b} \ S_{2a \cdot b})$ Poor contact and Short-circuit of the input terminal and pin jack.  C <sub>87</sub> , C <sub>122</sub> .
	A In case of small sounds on resp. AUX, FM (MPX), AM tuners, phono, tape recorder, mike etc.	In case there is something wrong in voltage in power circuit and resp. places.	Check the places where there is something wrong in voltage.
	A. In case of small sounds on AUX with nothing wrong in voltage in resp. places.	<ol> <li>Poor fixed resistor.</li> <li>Short-circuit rearing in the output transformer.</li> </ol>	Compound parts CRS-01, CRS-02, CRS-10A. T <sub>8</sub> , T <sub>9</sub>

When the		Symptoms (2)	Likely defective places
Power switch is pushed, electric supply is on.		Drop in condenser capacity and short-circuit.      Deterioration of vacuum tubes.	Insufficient capacity of $C_{90}$ , $C_{125}$ , $C_{92}$ , $C_{129}$ , $C_{99}$ , $C_{134}$ , $C_{111}$ , $C_{112}$ , $C_{145}$ , $C_{144}$ and tubular electrolytic condensers $C_{91}$ $C_{126}$ . $V_{14}{\sim}V_{21}$
_	B. In case of small FM broad- casting sounds with noth- ing wrong in voltage in	Divergence in tracking regulation.	Refer to the regulation method of the FM tuner.
	resp. places.	2. Divergence in IFT regulation.	Refer to the regulation method of the FM tuner.
		3. Poor diode.	Germanium diode (OA-91)
		4. Drop in Q of coils etc.	L <sub>1</sub> , L <sub>5</sub> , L <sub>6</sub>
		5. Poor condensers.	Insufficient capacity of C <sub>11</sub> , C <sub>14</sub> , C <sub>16</sub> , C <sub>41</sub> , C <sub>43</sub> .
		6. Misregulation of the semi-fixed resistors.	VR-1 VR-4
		7. Poor contact of the rotary switch.	$S_{2b}$
	C. In case of small sounds on the FM multiplex stereo	Insufficient capacity of the coupling condensers.	C <sub>45</sub> , C <sub>43</sub> , C <sub>53</sub> , C <sub>62</sub> , C <sub>64</sub> , C <sub>66</sub> , C <sub>67</sub>
	broadcasting with nothing wrong in voltage in resp.	2. Divergence in regulation of coils, etc.	$L_{10}$ , $L_{12}$ , $L_{13}$
	places.	3. Change in capacity of the condensers in the tank circuit.	C <sub>49</sub> , C <sub>55</sub> , C <sub>56</sub>
		4. Deterioration of diode.	Germanium diode OA-91
		5. Misregulation of the semi-fixed resistors.	VR-4, VR-5
<u></u>		6. Poor contact of the rotary switch.	$S_{2b}$
	D In case of small AM broad- casting sounds with noth-	1. Divergence in tracking regulation.	Refer to the regulation method of the AM tuner.
	ing wrong in voltage in resp. places.	2. Divergence in IFT regulation.	Refer to the regulation method of the AM tuner.
		3. Poor diode.	OA-91
		4. Drop in Q of coils, etc.	$L_7$ , $L_8$
		5. Poor condensers.	Insufficient capacity of C <sub>28</sub> , C <sub>16</sub> , C <sub>39</sub>
			$R_{32}, R_{35}$
		<ol><li>Misregulation of the semi-fixed resistor.</li></ol>	VR-4
-		7. Poor contact of the rotary switch.	$S_{2b}$
	E In case of small sounds on the phono, tape recording	1. In case of poor contact of the selector switch.	S <sub>1a</sub> , b, e, f
-	and mike with nothing wrong in voltage in resp. places.	2. In case there is something wrong in the input circuit.	Poor contact of the pin jack or poor shielded wires.
	,	3. Poor condition of the attached appliances connected.	
	ļ	4. Poor coupling condensers.	$C_{75}$ , $C_{84}$ , $C_{87}$ , $C_{114}$ , $C_{115}$ , $C_{112}$
		5. Insufficient capacity of emitter bypass condensers.	$C_{83}$ , $C_{85}$ , $C_{116}$ , $C_{120}$
	A. In case the sounds from	1. Deterioration of vacuum tubes.	V <sub>15</sub> , V <sub>19</sub>
	the AUX terminal are distorted much.	2. Partial short-circuit rearing in the output	$T_8$ , $T_9$
		transformer. 3. Poor speaker.	
		4. Distortion resulted from the attached	
		appliances connected.	

# SERVICE NOTE

	Symptoms (1)	Symptoms (2)	Likely defective places
When the Power switch is pushed, electric sup- ply is not on.	A. Poor power switch. B. Poor power cord. C. Poor plug contact. D. Blown fuse.	(In case the fuse blows again upon fitting a new one)	Replace it. Replace it. Replace the plug or make the plug contact better. Replace it. Short-circuit rearing in the power transformer (T <sub>10</sub> ) or short-circuit of path condenser (C <sub>149</sub> )
When the power switch is pushed, electric supply is on.	A. The amplifier does not work at all.	Broken wires of vacuum tube heaters.     In case there is something wrong in the vacuum tube and voltage in resp. places     In case there is nothing wrong in the vacuum tube and voltage in resp. places	$V_1 \sim V_{21}$ and silicon diodes. Check the places where there is something wrong in voltage. Check the input circuit after AUX.
	B. Only the FM tuner does not work at all.	<ol> <li>Broken wires of vacuum tube heaters in the FM system.</li> <li>In case there is something wrong in the vacuum tube and voltage in resp. places in the FM system.</li> <li>In case there is nothing wrong in resp. places in the FM system.</li> </ol>	V <sub>1</sub> ~V <sub>7</sub> , V <sub>10</sub> Check the places where there is something wrong in voltage.  Insufficient capacity of C <sub>42</sub> , C <sub>43</sub> . Poor IFT (T <sub>1</sub> ~T <sub>5</sub> ). Short-circuit of C <sub>25</sub> , C <sub>26</sub> , C <sub>27</sub> , C <sub>44</sub> . Trouble in the local oscillating circuit of V <sub>3b</sub> (6AQ8)
	C. Only the FM-MPX system does not work.	<ol> <li>Broken wires of vacuum tube heaters in the multiplex system.</li> <li>In case there is something wrong in the vacuum tube and voltage in resp. places in the multiplex system.</li> <li>In case there is nothing wrong in the vacuum tube and voltage in the multiplex system.</li> </ol>	If the FM tuner works normally, check $V_{11} \sim V_{13}$ . Check the places where there is something wrong in voltage.  If the FM tuner works normally, it is caused by insufficient capacity of $C_{45}$ , $C_{62}$ , $C_{64}$ , $C_{66}$ , $C_{67}$ , and poor $L_{10}$ , $L_{12}$ , $L_{13}$ .
	D. Only the AM tuner does not work	<ol> <li>Broken wires of vacuum tube heaters in the AM tuner system.</li> <li>In case there is something wrong in the vacuum tube and voltage in resp. places in the AM tuner system.</li> <li>In case there is nothing wrong in the vacuum tube and voltage in resp. places in the AM tuner system.</li> </ol>	V <sub>8</sub> , V <sub>9</sub> , V <sub>5</sub> Check the places where there is something wrong in voltage.  Poor IFT (T <sub>6</sub> , T <sub>7</sub> ) and RF coil (L <sub>8</sub> ). Poor diode (OA-91). Short-circuit of C <sub>18</sub> and C <sub>20</sub> . Insufficient capacity of C <sub>29</sub> .
	E. The phono, tape head and mike systems do not work.	<ol> <li>In case of poor TR head.</li> <li>In case of poor contact of the selector switch.</li> <li>In case there is something wrong in the input circuit.</li> <li>Poor condition of the attached appliances connected.</li> <li>Poor coupling condenser 0.05 μF.</li> </ol>	Replace the TR head amplifier unit.  Replace it or repair the contact (S <sub>1a·b</sub> S <sub>2a·b</sub> )  Poor contact and Short-circuit of the input terminal and pin jack.  C <sub>87</sub> , C <sub>122</sub> .
	A In case of small sounds on resp. AUX, FM (MPX), AM tuners, phono, tape recorder, mike etc.	In case there is something wrong in voltage in power circuit and resp. places.	Check the places where there is something wrong in voltage.
	A. In case of small sounds on AUX with nothing wrong in voltage in resp. places.	<ol> <li>Poor fixed resistor.</li> <li>Short-circuit rearing in the output transformer.</li> </ol>	Compound parts CRS-01, CRS-02, CRS-10A. T <sub>8</sub> , T <sub>9</sub>

# SERVICE NOTE

	Symptoms (1)	Symptoms (2)	Likely defective places
When the power switch is pushed, electric sup- ply is on.	B. In case the FM broadcasting sounds are distorted much.	<ol> <li>Poor condition and small input of the antenna.</li> <li>Divergence in tracking regulation.</li> <li>Divergence in regulation of IFT.</li> <li>Poor germanium diode.</li> <li>Insufficient capacity of the condensers in the FM tuner part.</li> </ol>	Refer to the item, How to install the antenna in this manual.  Refer to the regulation method of FM.  Refer to the regulation method of FM.  OA-91  C <sub>13</sub> , C <sub>15</sub> , C <sub>17</sub> , C <sub>21</sub> , C <sub>24</sub> , C <sub>35</sub>
	C. In case the sounds on the FM multiplex stereo broadcasting are distorted much.	<ol> <li>Sounds distorted at FM tuner.</li> <li>Poor regulation of the multiplex coil.</li> <li>Poor germanium diode.</li> <li>Poor condensers.</li> <li>Poor fixed resistor.</li> </ol>	Refer to the item B in Symptoms 1.  Refer to the regulation method of the multiplex adapter.  (OA-91)  Poor insulation of C <sub>62</sub> , C <sub>64</sub> Broken wires of R <sub>46</sub> , R <sub>55</sub> , R <sub>63</sub> , R <sub>67</sub>
	D. In case the AM broadcasting sounds are distorted much.	<ol> <li>Divergence in tracking regulation.</li> <li>Divergence in regulation of IFT.</li> <li>Poor germanium diode.</li> <li>Insufficient capacity of condenser and short-circuit.</li> </ol>	Refer to the regulation method of AM. Refer to the regulation method of AM. OA-91 Insufficient capacity of C <sub>29</sub> , C <sub>38</sub> . Puncture of C <sub>34</sub>
	E. In case the sounds on the phono, tape recording and mike are distorted much.	In case of much distortion in the attached appliances connected.     Poor tubular electrolytic condensers.	Puncture of C <sub>75</sub> and C <sub>114</sub>
	A. In case of big humming at the AUX terminal.	<ol> <li>Insufficient capacity of the electrolytic condensers.</li> <li>Inner touch of vacuum tubes.</li> <li>Big humming in the attached appliances connected.</li> <li>Poor regulation of the hum balancer.</li> <li>Broken wires of the NF resistors.</li> </ol>	$C_{156}$ , $C_{113}$ , $C_{108}$ $V_{14} \sim V_{21}$ $V_{14} \sim V_{11}$ $V_{14} \sim V_{14}$ $V_{14} \sim V_{14}$ $V_{14} \sim V_{14}$ $V_{14} \sim V_{14}$
	B. In case of big humming on the FM broadcasting.	Hums generated when tuned to a channel.     Inner touch of vacuum tubes.	Reverse connection of the power plug or poor earthing condition of the chassis. $V_1 \sim V_7$ , $V_{10}$
	C. In case of big humming on the FM multiplex circuit system.	Hums generated from the above-mentioned causes.      Inner touch of vacuum tubes.	Reverse connection of the power plug or poor earthing condition of the chassis. $V_1 \sim V_7$ , $V_{10} \sim V_{13}$
	D. In case of big humming on the AM broadcasting.	<ol> <li>Hums generated when tuned to a channel.</li> <li>Inner touch of vacuum tubes.</li> </ol>	Reverse connection of the power plug or poor earthing condition of the chassis. $V_8,\ V_9,\ V_5$
	E. In case of big humming on the phono, tape recording and mike systems.	<ol> <li>Poor condition of shielded wires with sound appliances and their connection.</li> <li>Sound appliances and the shielded wires are subjected to external induction.</li> <li>Residual hums of sound appliances.</li> </ol>	Refer to the item PRECAUTIONS in this manual.  Install them as far away as possible from the induction machines.

	Symptoms (1)	Symptoms (2)	Likely defective places
When the power switch is pushed, electric supply is on.	A. In case of loud noises at the AUX terminal.	<ol> <li>Break rearing in the fixed resistor wires and touch of parts.</li> <li>Short-circuit rearing at the condensers and touch of parts.</li> </ol>	$R_{100}$ , $R_{105}$ , $R_{115}$ , $R_{116}$ , $R_{119}$ , $R_{121}$ , $R_{149}$ , $R_{154}$ , $R_{164}$ , $R_{165}$ , $R_{167}$ , $R_{169}$ $C_{106}$ , $C_{109}$ , $C_{141}$ , $C_{142}$
. •		<ul><li>3. Break rearing in the primary side of the output transformers.</li><li>4. Inner touch of vacuum tubes.</li></ul>	$V_{14} \sim V_{21}$
	B. In case of a great many noise on the FM broad- casting.	<ol> <li>Small input voltage and poor condition of the antenna.</li> <li>Poor vacuum tubes (high howling)</li> <li>Break rearing in the fixed resistor wires and touching of parts.</li> <li>Short-circuit of condensers and touch of parts.</li> </ol>	Refer to the item ANTENNA in this manual. $V_1$ , $V_2$ , $V_3$ $R_2$ , $R_3$ , $R_5$ , $R_7$ , $R_9$ , $R_{12}$ , $R_{14}$ , $R_{15}$ , $R_{18}$ $C_3$ , $C_7$ , $C_{13}$ , $C_{15}$ , $C_{17}$ , $C_{21}$ , $C_{24}$
	C. In case of a great many noises on the FM multiplex stereo broadcasting.	<ol> <li>Noises made by the above-mentioned causes.</li> <li>Break rearing in the multiplex coil wires.</li> <li>Break rearing at the fixed resistors.</li> <li>Short-circuit rearing at condensers.</li> <li>Poor vacuum tubes.</li> </ol>	Refer to B. $L_{10}{\sim}L_{13}$ $R_{49}, R_{56}, R_{65}, R_{64}, R_{66}, R_{68}$ $C_{45}, C_{45}, C_{52}, C_{53}, C_{62}, C_{64}, C_{66}, C_{67}$ $V_{11}{\sim}V_{13}$
	D. In case of a great many noises on the phono, tape recording and mike systems.	<ol> <li>Poor condition of fixed resistors and break rearing at the resistor wires.</li> <li>Poor condensers.</li> <li>Inner noises and poor connection of the attached appliances connected.</li> </ol>	$R_{84} \sim R_{96}, R_{133} \sim R_{145}$ $C_{75} \sim C_{87}, C_{114} \sim C_{122}$
	A. While the FM tuner is working normally.	<ol> <li>The tuning meter does not work at all.</li> <li>The tuning meter works slightly.</li> </ol>	<ul> <li>Poor (M) and broken wire of R<sub>28</sub></li> <li>It varies depends on the intensity of the electric field resulted from regional differences.</li> <li>It is caused by poor condition of FM antenna.</li> </ul>
	B. While the AM tuner is working normally.	<ol> <li>The tuning meter does not work at all.</li> <li>The tuning meter works slightly.</li> <li>In case the zero point of the meter diverges much.</li> </ol>	<ul> <li>Poor (M) and broken wire of R<sub>10</sub>.</li> <li>It varies depending on the intensity of the electric field resulted from regional differences.</li> <li>Broken wires of R<sub>29</sub>, R<sub>30</sub>.</li> </ul>
	C. The stereo indicator is not lighted at the time of FM stereo reception.	<ol> <li>In case the multiplex adapter does not work normally.</li> <li>In case only the indicator does not work with the multiplex adapter working normally.</li> <li>The indicator is kept lighting while the multiplex adapter is working normally.</li> </ol>	Refer to the item Symptoms of respective Multiplex. Poor NL, broken wire of $R_{50}$ and poor $V_{11}$ . Poor OA-91 and poor regulation of VR-2.
	D. Poor separation at the time of FM stereo reception.	1. In case the multiplex adapter works normally.	Poor regulation of VR-3 (Refer to the regulation method of multiplex).



# ALIGNMENT

# FM ALIGNMENT PROCEDURE

AFC-OFF

2. Turn tuning gang fully

3. Center carrier wave.

4. Set pointer at reference mark.

1. AFC	C-OFF	<ol><li>Turn tuning gar</li></ol>	ng fully	<ol><li>Center carrier v</li></ol>	vave.	4. Set pointer at	reterence mark.
STEP	ALIGN	GENERATOR	FEED SIGNAL	OUTPUT INDICATOR	DIAL SETTING	ADJÜST	ADJUST FOR
1.	IF Transformer	10.7 MC ±400 KC	V <sub>6</sub> Pin 1 6AU6	oscilloscope at ①		4th IFT (T <sub>4</sub> ) Primary & Secondary	Best IFT Wave form
		10.7 MC ±400 KC	V <sub>5</sub> Pin 1 6BA6	oscilloscope at ①	÷	3rd IFT (T <sub>3</sub> ) Primary & Secondary	Best IFT Wave form
		10.7 MC ±400 KC	V₄ Pin 1 6BA6	oscilloscope at ①		2nd IFT (T <sub>2</sub> ) Primary & Secondary	Best IFT Wave form
		10.7 MC ±400 KC	Couple Sweep Signal by a round tube V <sub>3</sub> 6AQ8	oscilloscope at ①		1st IFT (T <sub>1</sub> ) Primary & Secondary	Best IFT Wave form
2.	Discrimi- nator	10.7 MC ±400 KC	Couple Sweep Signal by a round tube V <sub>3</sub> 6AQ8	oscilloscope at ②		5th IFT (T <sub>5</sub> ) Discriminator Transformer	S Curve
3.	OSC.	88 MC 400 c/s 100 % Modulation	Antenna Terminals	oscilloscope & V.T, V.M. at oscillo load	88 MC	OSC. coil L <sub>6</sub>	Maximum
4.	osc.	108 MC 400 c/s 100 % Modulation	Antenna Terminals	oscilloscope & V.T, V.M. at oscillo load	108 MC	OSC. Trimmer TC <sub>3</sub>	Maximum
5.		Reiterate 3, 4					
6.	RF Amp.	88 MC 400 c/s 100 <i>%</i> Modulation	Antenna Terminals	oscilloscope & V.T, V.M. at oscillo load	88 MC	RF Amp. coil L <sub>5</sub>	Maximum
7.	Antenna circuit	88 MC 400 c/s 100 <i>%</i> Modulation	Antenna Terminals	oscilloscope & V.T, V.M. at oscillo load	88 MC	Antenna coil L <sub>1</sub>	Maximum
8.	RF Amp	104 MC 400 c/s 100 <i>%</i> Modulation	Antenna Terminals	oscilloscope & V.T, V.M. at oscillo load	104 MC	RF. Amp Trimmer TC <sub>2</sub>	Maximum
9.	Antenna circuit	104 MC 400 c/s 100 <i>%</i> Modulation	Antenna Terminals	oscilloscope & V.T, V.M. at oscillo load	104 MC	Antenna circuit Trimmer TC <sub>1</sub>	Maximum
10.		Reiterate 6, 7, 8, 9					

STEP	ALIGN	GENERATOR	FEED SIGNAL	OUTPUT INDICATOR	DIAL SETTING	• ADJUST	ADJUST FOR
1.	IF Trans- former	455 KC ± 30 KC sweep-generator	Pin 7 6BE6	Sweep input at ③		1st I.F.T (T <sub>6</sub> ) Primary & Secondary 2nd I.F.T (T <sub>7</sub> ) Primary & Secondary	Best I.F.T Wave form
2.	OSC.	AM-OSCILLATOR 535 KC 400 c/s 30% Modulation	Antenna Terminals	oscilloscope & V.T, V.M. at output load	535 KC	OSC. coil L <sub>9</sub>	Maximum
3.	osc.	1605 KC 400 c/s 30 <i>%</i> Modulation	Antenna Terminals	oscilloscope & V.T, V.M. at output load	1605 KC	OSC. Trimmer · TC <sub>6</sub>	Maximum
4.		Reiterate 2, 3,					
5.	RF Amp.	600 KC 400 c/s 30% Modulation	Antenna Terminals	oscilloscope & V.T, V.M. at output load	600 KC	RF coil L <sub>8</sub>	Maximum
6.	RF Amp.	140 KC 400 c/s 30 <i>%</i> Modulation	Antenna Terminals	oscilloscope & V.T, V.M. at output load	1400 KC	RF Trimmer TC <sub>5</sub>	Maximum
7.		Reiterate 5, 6,					
8.	Antenna circuit	600 KC 400 c/s 30% Modulation	Antenna Terminals	oscilloscope & V.T, V.M. at output load	600 KC	Ferrite Loop Antenna at coil L <sub>7</sub>	Maximum
9.	Antenna	1400 KC 400 c/s 30 <i>%</i> Modulation		oscilloscope & V.T, V.M. at output load	1400 KC	Antenna circuit at Trimmer TC-4	Maximum
10.		Reiterate 8, 9.					

1. Do not attempt to align the Multiplex Circuit unless the following equipment is available:

a. Multiplex Stereo Generator b. FM Signal Generator c. Oscilloscope

d. Sweep Generator

e. AC V.T, V.M.

f. Audio oscillator

STEP	ALIGN	GENERATOR	FEED SIGNAL	OUTPUT INDICATOR	ADJUST	ADJUST FOR
1.	67 KC Trap	67 KC Audio Signal	Connect to T.P ④	V.T, V.M. at T.P ⑤	L <sub>11</sub>	Minimum
2.	19 KC coil Transformer	FM Signal Gen. Modulated 30% by Stereo Gen. sub-Channel	Antenna Terminals Tune to signal	V.T, V.M. & Oscilloscope at output load	$oxed{L_{10}}$	Maximum
3.	19 KC coil	Same	Same	Same	L <sub>12</sub>	Maximum
4.	38 KC Doubler	Same	Same	Same	L <sub>13</sub>	Maximum
5.	Separation VR	FM Signal Gen. Modulated 30% by Stereo Signal Gen. Channel-L	Same	V.T, V.M. & Oscilloscode at output load Channel-R	Separa- tion VR <sub>3</sub>	Channel-R Minimum



# PARTS LIST

Part No.		Ν	omenc	lature			
Rı	47 KΩ	½Watt	10%	Carbon	Fixed	Resistor	
R <sub>2</sub>	1.5 ΚΩ	½ Watt	10%	Carbon	Fixed	Resistor	
R3	3.3 KΩ	½ Watt	10%	Carbon	Fixed	Resistor	
R4	$\Omega$ 86	1/4 Watt	10%	Carbon	Fixed	Resistor	
R5	- 1 KΩ	1/4Watt	10%	Carbon	Fixed	Resistor	
R6	1.5 K $\Omega$	½Watt	10%	Carbon	Fixed	Resistor	
<b>R</b> 7	1 ΚΩ	1/4 Watt	10%	Carbon	Fixed	Resistor	
R8	68 Ω	1/4 Watt	10%	Carbon	Fixed	Resistor	
R9	1 ΚΩ 4 ΚΩ	½Watt	10%	Carbon Carbon	Fixed Fixed	Resistor Resistor	
R10 R11	68 Ω	¼Watt ¼Watt	10% 10%	Carbon	Fixed	Resistor	
R12	1 ΚΩ	½ Watt	10%	Carbon	Fixed	Resistor	
R13	40 KΩ	1/4 Watt	10%	Carbon	Fixed	Resistor	
R14	15 K $\Omega$	1 Watt	10%	Carbon	Fixed	Resistor	
R15	15 K $\Omega$	2 Watt	10%	Carbon	Fixed	Resistor	
R16	3 M $\Omega$	1/4 Watt	10%	Carbon	Fixed	Resistor	
R17	68 KΩ	1/4Watt	10%	Carbon	Fixed	Resistor	
R18	20 ΚΩ	½Watt	10%	Carbon Carbon	Fixed	Resistor Resistor	
R19 R20	1 ΚΩ 1 ΚΩ	⅓Watt ⅓Watt	10% 10%	Carbon	Fixed Fixed	Resistor	
R21	$1 M\Omega$	1/4 Watt	10%	Carbon	Fixed	Resistor	
R22	100 Ω	1/4 Watt	10%	Carbon	Fixed	Resistor	
R23	20 KΩ	½ Watt	10%	Carbon	Fixed	Resistor	
R24	20 K $\Omega$	1/4 Watt	10%	Carbon	Fixed	Resistor	
R25	50 $\Omega$	¼Watt	10%	Carbon	Fixed	Resistor	
R26	8 KΩ	1 Watt	10%	Carbon	Fixed	Resistor	
R27	2 MΩ	1/4Watt	10%	Carbon	Fixed	Resistor	
R28	47 ΚΩ 500 Ω	¼Watt ¼Watt	10% 10%	Carbon Carbon	Fixed Fixed	Resistor Resistor	
R29 R31	300,42 10 KΩ	¼ vvatt ¼Watt	10%	Carbon	Fixed	Resistor	
R32	100 KΩ	1/4 Watt	10%	Carbon	Fixed	Resistor	
R33	2.2 M $\Omega$	½ Watt	10%	Carbon	Fixed	Resistor	
R34	100 K $\Omega$	1/4 Watt	10%	Carbon	Fixed	Resistor	
R35	50 K $\Omega$	¼Watt	10%	Carbon	Fixed	Resistor	
R36	2 ΜΩ	1/4 Watt	10%	Carbon	Fixed	Resistor	
R37	$2.2\mathrm{M}\Omega$	1/4 Watt	10%	Carbon	Fixed	Resistor	
R38 R39	220 KΩ 500 KΩ	½Watt ⅓Watt	10% 10%	Carbon Carbon	Fixed Fixed	Resistor Resistor	
R40	50 KΩ	1/4 Watt	10%	Carbon	Fixed	Resistor	
R41	7 ΚΩ	1/4 Watt	10%	Carbon	Fixed	Resistor	
R42	1 M $\Omega$	1/4 Watt	10%	Carbon	Fixed	Resistor	
R43	50 K $\Omega$	$\frac{1}{2}$ Watt	10%	Carbon	Fixed	Resistor	
R44	82 KΩ	1/4Watt	10%	Carbon	Fixed	Resistor	
R45	1 ΚΩ	1/4 Watt	10%	Carbon	Fixed	Resistor	
R46	510 KΩ	1/4 Watt	10%	Carbon	Fixed	Resistor	
R47 R48	4.7 KΩ 470 Ω	⅓Watt ⅓Watt	10% 10%	Carbon Carbon	Fixed Fixed	Resistor Resistor	
R49	10 KΩ	½ Watt	10%	Carbon	Fixed	Resistor	
R50	150 KΩ	½Watt	10%	Carbon	Fixed	Resistor	
R51	200 K $\Omega$	$\frac{1}{2}$ Watt	10%	Carbon	Fixed	Resistor	
R52	2.2 M $\Omega$	1/4 Watt	10%	Carbon	Fixed	Resistor	
R53	1 KΩ	1/4 Watt	10%	Carbon	Fixed	Resistor	
R54	1 KΩ	1/4 Watt	10%	Carbon	Fixed	Resistor	
R55 R56	510 KΩ 100 KΩ	¼Watt ½Watt	10% 10%	Carbon Carbon	Fixed Fixed	Resistor Resistor	
R56	39 KΩ	1/4 Watt	10%	Carbon	Fixed	Resistor	
R58	10 KΩ	1/4 Watt	10%	Carbon	Fixed	Resistor	
R59	47 KΩ	1/4 Watt	10%	Carbon	Fixed	Resistor	
<b>R</b> 60	47 K $\Omega$	1/4 Watt	10%	Carbon	Fixed	Resistor	
R61	47 K $\Omega$	1/4 Watt	10%	Carbon	Fixed	Resistor	
R62	47 KΩ	1/4 Watt	10%	Carbon	Fixed	Resistor	
R63	10 MΩ	1/2 Watt	10%	Carbon	Fixed	Resistor	
R64	15 KΩ 22 KΩ	½Watt ½Watt	10% 10%	Carbon Carbon	Fixed Fixed	Resistor Resistor	
R65 R66	15 KΩ	½ Watt	10%	Carbon	Fixed	Resistor	
Koo	,5,7,4,2	/4,,,,,,,,,,,,,,,,,,,,,,,,,,,,,,,,,,,,,	, = / 5				

R67				•				
R68         22 KΩ         ½ Watt         10%         Carbon         Fixed         Resistor           R70         51 KΩ         ½ Watt         10%         Carbon         Fixed         Resistor           R71         10 KΩ         ½ Watt         10%         Carbon         Fixed         Resistor           R71         10 KΩ         ½ Watt         10%         Carbon         Fixed         Resistor           R72         2.2 KΩ         ½ Watt         10%         Carbon         Fixed         Resistor           R73         10 KΩ         ½ Watt         10%         Carbon         Fixed         Resistor           R74         51 KΩ         ½ Watt         10%         Carbon         Fixed         Resistor           R76         8.2 KΩ         ½ Watt         10%         Carbon         Fixed         Resistor           R77         100 KΩ         ¼ Watt         10%         Carbon         Fixed         Resistor           R78         100 KΩ         ¼ Watt         10%         Carbon         Fixed         Resistor           R81         150 KΩ         ¼ Watt         10%         Carbon         Fixed         Resistor           R83         150 K	Part No.		No	omen	clature			
R68         22 KΩ         ½ Watt         10%         Carbon         Fixed         Resistor           R70         51 KΩ         ½ Watt         10%         Carbon         Fixed         Resistor           R71         10 KΩ         ½ Watt         10%         Carbon         Fixed         Resistor           R71         10 KΩ         ½ Watt         10%         Carbon         Fixed         Resistor           R72         2.2 KΩ         ½ Watt         10%         Carbon         Fixed         Resistor           R73         10 KΩ         ½ Watt         10%         Carbon         Fixed         Resistor           R74         51 KΩ         ½ Watt         10%         Carbon         Fixed         Resistor           R76         8.2 KΩ         ½ Watt         10%         Carbon         Fixed         Resistor           R77         100 KΩ         ¼ Watt         10%         Carbon         Fixed         Resistor           R78         100 KΩ         ¼ Watt         10%         Carbon         Fixed         Resistor           R81         150 KΩ         ¼ Watt         10%         Carbon         Fixed         Resistor           R83         150 K	Dizz	1040	1/14/	100/	C 1	F1 d	Desistan	
R69			· -					
R70			·					
R71								
R73	<b>R</b> 71	10 K $\Omega$					Resistor	
R74	R72	2.2 K $\Omega$		10%	Carbon	Fixed	Resistor	
R75	i	10 KΩ		10%	Carbon	Fixed	Resistor	
R/6 8.2 KΩ $\frac{1}{4}$ Watt 10% Carbon Fixed Resistor R/7 100 KΩ $\frac{1}{4}$ Watt 10% Carbon Fixed Resistor R/7 800 KΩ $\frac{1}{4}$ Watt 10% Carbon Fixed Resistor R/7 800 KΩ $\frac{1}{4}$ Watt 10% Carbon Fixed Resistor R/8 150 KΩ $\frac{1}{4}$ Watt 10% Carbon Fixed Resistor R/8 150 KΩ $\frac{1}{4}$ Watt 10% Carbon Fixed Resistor R/8 150 KΩ $\frac{1}{4}$ Watt 10% Noise Less Resistor R/8 150 KΩ $\frac{1}{4}$ Watt 10% Noise Less Resistor R/8 150 KΩ $\frac{1}{4}$ Watt 10% Noise Less Resistor R/8 150 KΩ $\frac{1}{4}$ Watt 10% Noise Less Resistor R/8 150 KΩ $\frac{1}{4}$ Watt 10% Noise Less Resistor R/8 150 KΩ $\frac{1}{4}$ Watt 10% Noise Less Resistor R/8 150 $\frac{1}{4}$ Watt 10% Noise Less Resistor R/9 150 $\frac{1}{4}$ Watt 10% Noise Less Resistor R/9 150 $\frac{1}{4}$ Watt 10% Noise Less Resistor R/9 150 $\frac{1}{4}$ Watt 10% Carbon Fixed Resistor R/9 120 $\frac$			· . · .			Fixed		
R77	,		7 "					
R78			*. *.					
R79 800 KΩ $\frac{1}{N}$ Worth 10% Carbon Fixed Resistor R81 150 KΩ $\frac{1}{N}$ Worth 10% Carbon Fixed Resistor R84 100 KΩ $\frac{1}{N}$ Worth 10% Noise Less Resistor R85 170 KΩ $\frac{1}{N}$ Worth 10% Noise Less Resistor R85 170 KΩ $\frac{1}{N}$ Worth 10% Noise Less Resistor R85 15 KΩ $\frac{1}{N}$ Worth 10% Noise Less Resistor R87 300 Ω $\frac{1}{N}$ Worth 10% Noise Less Resistor R88 15 KΩ $\frac{1}{N}$ Worth 10% Noise Less Resistor R89 70 KΩ $\frac{1}{N}$ Worth 10% Noise Less Resistor R89 70 KΩ $\frac{1}{N}$ Worth 10% Noise Less Resistor R91 16 KΩ $\frac{1}{N}$ Worth 10% Carbon Fixed Resistor R91 16 KΩ $\frac{1}{N}$ Worth 10% Carbon Fixed Resistor R93 12 KΩ $\frac{1}{N}$ Worth 10% Carbon Fixed Resistor R94 3 KΩ $\frac{1}{N}$ Worth 10% Carbon Fixed Resistor R95 10 Ω $\frac{1}{N}$ Worth 10% Carbon Fixed Resistor R96 12 KΩ $\frac{1}{N}$ Worth 10% Carbon Fixed Resistor R97 40 KΩ $\frac{1}{N}$ Worth 10% Carbon Fixed Resistor R96 500 KΩ $\frac{1}{N}$ Worth 10% Carbon Fixed Resistor R97 40 KΩ $\frac{1}{N}$ Worth 10% Carbon Fixed Resistor R97 40 KΩ $\frac{1}{N}$ Worth 10% Carbon Fixed Resistor R96 500 KΩ $\frac{1}{N}$ Worth 10% Carbon Fixed Resistor R97 2 KΩ $\frac{1}{N}$ Worth 10% Carbon Fixed Resistor R97 2 KΩ $\frac{1}{N}$ Worth 10% Carbon Fixed Resistor R98 500 KΩ $\frac{1}{N}$ Worth 10% Carbon Fixed Resistor R100 50 KΩ $\frac{1}{N}$ Worth 10% Carbon Fixed Resistor R101 100 KΩ Enclosed in CRSO 2 R102 15 KΩ Enclosed in CRSO 2 R103 100 KΩ Enclosed in CRSO 2 R104 2 KΩ $\frac{1}{N}$ Worth 10% Carbon Fixed Resistor R105 50 KΩ $\frac{1}{N}$ Worth 10% Carbon Fixed Resistor R110 50 KΩ Enclosed in CRSO-1 R111 50 KΩ Enclosed in CRSO-1 R112 40 KΩ $\frac{1}{N}$ Worth 10% Carbon Fixed Resistor R113 100 Ω $\frac{1}{N}$ Worth 10% Carbon Fixed Resistor R114 1 KΩ $\frac{1}{N}$ Worth 10% Carbon Fixed Resistor R115 50 KΩ Enclosed in CRSO-1 R112 40 KΩ $\frac{1}{N}$ Worth 10% Carbon Fixed Resistor R116 150 KΩ $\frac{1}{N}$ Worth 10% Carbon Fixed Resistor R119 30 KΩ $\frac{1}{N}$ Worth 10% Carbon Fixed Resistor R119 30 KΩ $\frac{1}{N}$ Worth 10% Carbon Fixed Resistor R119 30 KΩ $\frac{1}{N}$ Worth 10% Carbon Fixed Resistor R120 50 KΩ $\frac{1}{N}$ Worth 10% Carbon Fixed	i e		1. 1.					
R81 150 K $\Omega$ $\frac{1}{4}$ Watt 10% Carbon Fixed Resistor R83 150 K $\Omega$ $\frac{1}{4}$ Watt 10% Noise Less Resistor R85 170 K $\Omega$ $\frac{1}{4}$ Watt 10% Noise Less Resistor R86 15 K $\Omega$ $\frac{1}{4}$ Watt 10% Noise Less Resistor R87 300 $\Omega$ $\frac{1}{4}$ Watt 10% Noise Less Resistor R87 300 $\Omega$ $\frac{1}{4}$ Watt 10% Noise Less Resistor R88 15 K $\Omega$ $\frac{1}{4}$ Watt 10% Noise Less Resistor R89 70 K $\Omega$ $\frac{1}{4}$ Watt 10% Noise Less Resistor R89 70 K $\Omega$ $\frac{1}{4}$ Watt 10% Noise Less Resistor R89 15 K $\Omega$ $\frac{1}{4}$ Watt 10% Noise Less Resistor R91 16 K $\Omega$ $\frac{1}{4}$ Watt 10% Noise Less Resistor R92 5 K $\Omega$ $\frac{1}{4}$ Watt 10% Carbon Fixed Resistor R93 12 K $\Omega$ $\frac{1}{4}$ Watt 10% Carbon Fixed Resistor R94 3 K $\Omega$ $\frac{1}{4}$ Watt 10% Carbon Fixed Resistor R95 10 $\Omega$ $\frac{1}{4}$ Watt 10% Noise Less Resistor R95 10 $\Omega$ $\frac{1}{4}$ Watt 10% Carbon Fixed Resistor R96 12 K $\Omega$ $\frac{1}{4}$ Watt 10% Carbon Fixed Resistor R97 40 K $\Omega$ $\frac{1}{4}$ Watt 10% Carbon Fixed Resistor R98 500 K $\Omega$ $\frac{1}{4}$ Watt 10% Carbon Fixed Resistor R99 2 K $\Omega$ $\frac{1}{4}$ Watt 10% Carbon Fixed Resistor R99 2 K $\Omega$ $\frac{1}{4}$ Watt 10% Carbon Fixed Resistor R100 50 K $\Omega$ $\frac{1}{4}$ Watt 10% Carbon Fixed Resistor R101 100 K $\Omega$ Enclosed in CRSO 2 R102 15 K $\Omega$ Enclosed in CRSO 2 R103 100 K $\Omega$ Enclosed in CRSO 2 R104 2 K $\Omega$ $\frac{1}{4}$ Watt 10% Carbon Fixed Resistor R105 50 K $\Omega$ $\frac{1}{4}$ Watt 10% Carbon Fixed Resistor R106 2 M $\Omega$ Enclosed in CRSO-1 R107 2 M $\Omega$ Enclosed in CRSO-1 R108 R119 50 K $\Omega$ Enclosed in CRSO-1 R110 R111 50 K $\Omega$ Enclosed in CRSO-1 R111 50 K $\Omega$ Enclosed in CRSO-1 R112 40 K $\Omega$ $\frac{1}{4}$ Watt 10% Carbon Fixed Resistor R113 100 $\Omega$ $\frac{1}{4}$ Watt 10% Carbon Fixed Resistor R114 1 K $\Omega$ $\frac{1}{4}$ Watt 10% Carbon Fixed Resistor R115 50 K $\Omega$ Enclosed in CRSO-1 R112 R112 40 K $\Omega$ $\frac{1}{4}$ Watt 10% Carbon Fixed Resistor R113 100 K $\Omega$ $\frac{1}{4}$ Watt 10% Carbon Fixed Resistor R114 15 K $\Omega$ $\frac{1}{4}$ Watt 10% Carbon Fixed Resistor R115 15 K $\Omega$ $\frac{1}{4}$ Watt 10% Carbon Fixed Resistor R119 30 K $\Omega$ $\frac{1}{4}$ Watt 10% Carbon Fixed Resistor R122 200 K $\Omega$ $\frac{1}{4}$	ł							
R83			7. 7.					
R84         100 KΩ         ¼Watt         10%         Noise         Less         Resistor           R85         170 KΩ         ¼Watt         10%         Noise         Less         Resistor           R87         300 Ω         ¼Watt         10%         Noise         Less         Resistor           R88         15 KΩ         ¼Watt         10%         Noise         Less         Resistor           R89         70 KΩ         ¼Watt         10%         Noise         Less         Resistor           R90         15 KΩ         ¼Watt         10%         Carbon         Fixed         Resistor           R91         16 KΩ         ¼Watt         10%         Carbon         Fixed         Resistor           R92         5 KΩ         ¼Watt         10%         Carbon         Fixed         Resistor           R92         5 KΩ         ¼Watt         10%         Carbon         Fixed         Resistor           R92         5 KΩ         ¼Watt         10%         Carbon         Fixed         Resistor           R94         3 KΩ         ¼Watt         10%         Carbon         Fixed         Resistor           R95         10 Ω         ½Watt			T. T.					
R85							2	
R86			5.5					
R87	l							
R88	i .							
R90	R88	15 K $\Omega$			Noise	Less	Resistor	
R91	<b>R</b> 89	70 K $\Omega$	1/4 Watt	10%	Noise	Less	Resistor	
R92 $5$ KΩ $\frac{1}{4}$ Watt $10\%$ Carbon Fixed ResistorR93 $12$ KΩ $\frac{1}{4}$ Watt $10\%$ Carbon Fixed ResistorR94 $3$ KΩ $\frac{1}{4}$ Watt $10\%$ Noise Less ResistorR95 $10$ Ω $\frac{1}{4}$ Watt $10\%$ Carbon Fixed ResistorR96 $12$ KΩ $\frac{1}{4}$ Watt $10\%$ Carbon Fixed ResistorR97 $40$ KΩ $\frac{1}{4}$ Watt $10\%$ Carbon Fixed ResistorR98 $500$ KΩ $\frac{1}{4}$ Watt $10\%$ Carbon Fixed ResistorR100 $50$ KΩ $\frac{1}{4}$ Watt $10\%$ Carbon Fixed ResistorR101 $100$ KΩEnclosed in CRSO 2ResistorR102 $15$ KΩEnclosed in CRSO 2R103 $100$ KΩEnclosed in CRSO 2R104 $2$ KΩ $\frac{1}{4}$ Watt $10\%$ Carbon Fixed ResistorR105 $50$ KΩ $\frac{1}{4}$ Watt $10\%$ Carbon Fixed ResistorR106 $2$ MΩEnclosed in CRSO-1R107 $2$ MΩEnclosed in CRSO-1R108 $1$ MΩEnclosed in CRSO-1R110 $50$ KΩEnclosed in CRSO-1R111 $50$ KΩEnclosed in CRSO-1R111 $50$ KΩEnclosed in CRSO-1R112 $40$ KΩ $\frac{1}{4}$ Watt $10\%$ Carbon Fixed ResistorR113 $100$ Ω $\frac{1}{4}$ Watt $10\%$ Carbon Fixed ResistorR114 $1$ KΩ $\frac{1}{4}$ Watt $10\%$ Carbon Fixed ResistorR115 $600$ KΩ $\frac{1}{4}$ Watt $10\%$ Carbon Fixed Resistor<	<b>R</b> 90	15 k $\Omega$	1/4 Watt	10%	Noise	Less	Resistor	
R93	R91			10%	Carbon	Fixed	Resistor	
R94 3 KΩ $\frac{1}{4}$ Watt 10% Noise Less Resistor R95 10 Ω $\frac{1}{4}$ Watt 10% Carbon Fixed Resistor R96 12 KΩ $\frac{1}{4}$ Watt 10% Noise Less Resistor R97 40 KΩ $\frac{1}{4}$ Watt 10% Carbon Fixed Resistor R97 40 KΩ $\frac{1}{4}$ Watt 10% Carbon Fixed Resistor R98 500 KΩ $\frac{1}{4}$ Watt 10% Carbon Fixed Resistor R99 2 KΩ $\frac{1}{4}$ Watt 10% Carbon Fixed Resistor R100 50 KΩ $\frac{1}{2}$ Watt 10% Noise Less Resistor R101 100 KΩ Enclosed in CRSO 2 R102 15 KΩ Enclosed in CRSO 2 R103 100 KΩ Enclosed in CRSO 2 R104 2 KΩ $\frac{1}{4}$ Watt 10% Carbon Fixed Resistor R105 50 KΩ $\frac{1}{2}$ Watt 10% Carbon Fixed Resistor R106 2 MΩ Enclosed in CRSO 100 KΩ Enclosed					Carbon	Fixed		•
R95					Carbon	Fixed	Resistor	
R96	i e							
R97 $40  \mathrm{K} \Omega$ $\frac{1}{4}  \mathrm{Watt}$ $10\%  \mathrm{Carbon}$ Fixed Resistor R98 $500  \mathrm{K} \Omega$ $\frac{1}{4}  \mathrm{Watt}$ $10\%  \mathrm{Carbon}$ Fixed Resistor R100 $50  \mathrm{K} \Omega$ $\frac{1}{4}  \mathrm{Watt}$ $10\%  \mathrm{Carbon}$ Fixed Resistor R100 $50  \mathrm{K} \Omega$ $\frac{1}{2}  \mathrm{Watt}$ $10\%  \mathrm{Carbon}$ Fixed Resistor R100 $50  \mathrm{K} \Omega$ $\frac{1}{2}  \mathrm{Watt}$ $10\%  \mathrm{Carbon}$ Fixed Resistor R101 $100  \mathrm{K} \Omega$ Enclosed in CRSO 2 R102 $15  \mathrm{K} \Omega$ Enclosed in CRSO 2 R103 $100  \mathrm{K} \Omega$ Enclosed in CRSO 2 R104 $2  \mathrm{K} \Omega$ $\frac{1}{4}  \mathrm{Watt}$ $10\%  \mathrm{Carbon}$ Fixed Resistor R105 $50  \mathrm{K} \Omega$ $\frac{1}{2}  \mathrm{Watt}$ $10\%  \mathrm{Carbon}$ Fixed Resistor R106 $2  \mathrm{M} \Omega$ Enclosed in CRS-10A R108 $1  \mathrm{M} \Omega$ Enclosed in CRS-10A R109 $50  \mathrm{K} \Omega$ Enclosed in CRS-10A R109 $50  \mathrm{K} \Omega$ Enclosed in CRSO-1 R110 $50  \mathrm{K} \Omega$ Enclosed in CRSO-1 R111 $50  \mathrm{K} \Omega$ Enclosed in CRSO-1 R112 $40  \mathrm{K} \Omega$ $\frac{1}{2}  \mathrm{Watt}$ $10\%  \mathrm{Carbon}$ Fixed Resistor R114 $1  \mathrm{K} \Omega$ $\frac{1}{2}  \mathrm{Watt}$ $10\%  \mathrm{Carbon}$ Fixed Resistor R115 $600  \mathrm{K} \Omega$ $\frac{1}{2}  \mathrm{Watt}$ $10\%  \mathrm{Carbon}$ Fixed Resistor R116 $150  \mathrm{K} \Omega$ $\frac{1}{2}  \mathrm{Watt}$ $10\%  \mathrm{Carbon}$ Fixed Resistor R117 $1.5  \mathrm{K} \Omega$ $\frac{1}{2}  \mathrm{Watt}$ $10\%  \mathrm{Carbon}$ Fixed Resistor R118 $15  \mathrm{K} \Omega$ $\frac{1}{2}  \mathrm{Watt}$ $10\%  \mathrm{Carbon}$ Fixed Resistor R119 $30  \mathrm{K} \Omega$ $\frac{1}{2}  \mathrm{Watt}$ $10\%  \mathrm{Carbon}$ Fixed Resistor R120 $50  \mathrm{K} \Omega$ $\frac{1}{2}  \mathrm{Watt}$ $10\%  \mathrm{Carbon}$ Fixed Resistor R121 $30  \mathrm{K} \Omega$ $\frac{1}{2}  \mathrm{Watt}$ $10\%  \mathrm{Carbon}$ Fixed Resistor R122 $3  \mathrm{K} \Omega$ $\frac{1}{2}  \mathrm{Watt}$ $10\%  \mathrm{Carbon}$ Fixed Resistor R123 $200  \mathrm{K} \Omega$ $\frac{1}{2}  \mathrm{Watt}$ $10\%  \mathrm{Carbon}$ Fixed Resistor R124 $200  \mathrm{K} \Omega$ $\frac{1}{2}  \mathrm{Watt}$ $10\%  \mathrm{Carbon}$ Fixed Resistor R125 $1  \mathrm{K} \Omega$ $\frac{1}{2}  \mathrm{Watt}$ $10\%  \mathrm{Carbon}$ Fixed Resistor R126 $1  \mathrm{K} \Omega$ $\frac{1}{2}  \mathrm{Watt}$ $10\%  \mathrm{Carbon}$ Fixed Resistor R127 $6  \mathrm{K} \Omega$ $\frac{1}{2}  \mathrm{Watt}$ $10\%  \mathrm{Carbon}$ Fixed Resistor R128 $3  \mathrm{K} \Omega$ $\frac{1}{2}  \mathrm{Watt}$ $10\%  \mathrm{Carbon}$ Fixed Resistor R128 $3  \mathrm{K}$	i .							
R98 $500  \mathrm{K}  \Omega$ $\frac{1}{4}  \mathrm{Watt}$ $10\%  \mathrm{Carbon}$ FixedResistorR99 $2  \mathrm{K}  \Omega$ $\frac{1}{4}  \mathrm{Watt}$ $10\%  \mathrm{Carbon}$ FixedResistorR100 $50  \mathrm{K}  \Omega$ $\frac{1}{2}  \mathrm{Watt}$ $10\%  \mathrm{Noise}$ LessResistorR101 $100  \mathrm{K}  \Omega$ Enclosedin CRSO 22R102 $15  \mathrm{K}  \Omega$ Enclosedin CRSO 22R103 $100  \mathrm{K}  \Omega$ Enclosedin CRSO 2R104 $2  \mathrm{K}  \Omega$ $\frac{1}{2}  \mathrm{Watt}$ $10\%  \mathrm{Carbon}$ FixedResistorR105 $50  \mathrm{K}  \Omega$ Enclosedin CRS-10AR106 $2  \mathrm{M}  \Omega$ Enclosedin CRS-10AR107 $2  \mathrm{M}  \Omega$ Enclosedin CRS-10AR108 $1  \mathrm{M}  \Omega$ Enclosedin CRS-10AR109 $50  \mathrm{K}  \Omega$ Enclosedin CRSO-1R110 $50  \mathrm{K}  \Omega$ Enclosedin CRSO-1R111 $50  \mathrm{K}  \Omega$ Enclosedin CRSO-1R112 $40  \mathrm{K}  \Omega$ $\frac{1}{2}  \mathrm{Watt}$ $10\%  \mathrm{Carbon}$ FixedResistorR113 $100  \Omega$ $\frac{1}{2}  \mathrm{Watt}$ $10\%  \mathrm{Carbon}$ FixedResistorR114 $1  \mathrm{K}  \Omega$ $\frac{1}{2}  \mathrm{Watt}$ $10\%  \mathrm{Carbon}$ FixedResistorR115 $600  \mathrm{K}  \Omega$ $\frac{1}{2}  \mathrm{Watt}$ $10\%  \mathrm{Carbon}$ FixedResistorR116 $150  \mathrm{K}  \Omega$ $\frac{1}{2}  \mathrm{Watt}$ $10\%  \mathrm{Carbon}$ FixedResistorR119 $30  \mathrm{K}  $			, .					
R99								
R100 $50  \mathrm{K}  \Omega$ $\frac{1}{2}  \mathrm{Watt}$ $10  \%$ Noise Less Resistor R101 $100  \mathrm{K}  \Omega$ Enclosed in CRSO 2 R102 $15  \mathrm{K}  \Omega$ Enclosed in CRSO 2 R103 $100  \mathrm{K}  \Omega$ Enclosed in CRSO 2 R104 $2  \mathrm{K}  \Omega$ $\frac{1}{2}  \mathrm{Watt}$ $10  \%$ Carbon Fixed Resistor R105 $50  \mathrm{K}  \Omega$ $\frac{1}{2}  \mathrm{Watt}$ $10  \%$ Carbon Fixed Resistor R106 $2  \mathrm{M}  \Omega$ Enclosed in CRS-10A R107 $2  \mathrm{M}  \Omega$ Enclosed in CRS-10A R108 $1  \mathrm{M}  \Omega$ Enclosed in CRS-10A R109 $50  \mathrm{K}  \Omega$ Enclosed in CRS-0-1 R110 $50  \mathrm{K}  \Omega$ Enclosed in CRSO-1 R111 $50  \mathrm{K}  \Omega$ Enclosed in CRSO-1 R112 $40  \mathrm{K}  \Omega$ $\frac{1}{2}  \mathrm{Watt}$ $10  \%$ Carbon Fixed Resistor R113 $100  \Omega$ $\frac{1}{2}  \mathrm{Watt}$ $10  \%$ Carbon Fixed Resistor R114 $1  \mathrm{K}  \Omega$ $\frac{1}{2}  \mathrm{Watt}$ $10  \%$ Carbon Fixed Resistor R115 $600  \mathrm{K}  \Omega$ $\frac{1}{2}  \mathrm{Watt}$ $10  \%$ Carbon Fixed Resistor R116 $150  \mathrm{K}  \Omega$ $\frac{1}{2}  \mathrm{Watt}$ $10  \%$ Carbon Fixed Resistor R118 $15  \mathrm{K}  \Omega$ $\frac{1}{2}  \mathrm{Watt}$ $10  \%$ Carbon Fixed Resistor R119 $30  \mathrm{K}  \Omega$ $\frac{1}{2}  \mathrm{Watt}$ $10  \%$ Carbon Fixed Resistor R120 $50  \mathrm{K}  \Omega$ $\frac{1}{2}  \mathrm{Watt}$ $10  \%$ Carbon Fixed Resistor R121 $30  \mathrm{K}  \Omega$ $\frac{1}{2}  \mathrm{Watt}$ $10  \%$ Carbon Fixed Resistor R122 $3  \mathrm{K}  \Omega$ $\frac{1}{2}  \mathrm{Watt}$ $10  \%$ Carbon Fixed Resistor R123 $200  \mathrm{K}  \Omega$ $\frac{1}{2}  \mathrm{Watt}$ $10  \%$ Carbon Fixed Resistor R124 $200  \mathrm{K}  \Omega$ $\frac{1}{2}  \mathrm{Watt}$ $10  \%$ Carbon Fixed Resistor R125 $1  \mathrm{K}  \Omega$ $\frac{1}{2}  \mathrm{Watt}$ $10  \%$ Carbon Fixed Resistor R126 $1  \mathrm{K}  \Omega$ $\frac{1}{2}  \mathrm{Watt}$ $10  \%$ Carbon Fixed Resistor R126 $1  \mathrm{K}  \Omega$ $\frac{1}{2}  \mathrm{Watt}$ $10  \%$ Carbon Fixed Resistor R126 $1  \mathrm{K}  \Omega$ $\frac{1}{2}  \mathrm{Watt}$ $10  \%$ Carbon Fixed Resistor R126 $1  \mathrm{K}  \Omega$ $\frac{1}{2}  \mathrm{Watt}$ $10  \%$ Carbon Fixed Resistor R127 $1  \mathrm{K}  \Omega$ $\frac{1}{2}  \mathrm{Watt}$ $10  \%$ Carbon Fixed Resistor R128 $1  \mathrm{K}  \Omega$ $\frac{1}{2}  \mathrm{Watt}$ $10  \%$ Carbon Fixed Resistor R129 $1  \mathrm{K}  \Omega$ $\frac{1}{2}  \mathrm{Watt}$ $10  \%$ Carbon Fixed Resistor R129 $1  \mathrm{K}  \Omega$ $\frac{1}{2}  \mathrm{Watt}$			1. 1.					
R101 $100  \mathrm{K} \Omega$ Enclosed in CRSO 2 R102 $15  \mathrm{K} \Omega$ Enclosed in CRSO 2 R103 $100  \mathrm{K} \Omega$ Enclosed in CRSO 2 R104 $2  \mathrm{K} \Omega$ $\frac{1}{2}  \mathrm{Watt}$ $10\%$ Carbon Fixed Resistor R105 $50  \mathrm{K} \Omega$ $\frac{1}{2}  \mathrm{Watt}$ $10\%$ Carbon Fixed Resistor R106 $2  \mathrm{M} \Omega$ Enclosed in CRS-10A R107 $2  \mathrm{M} \Omega$ Enclosed in CRS-10A R108 $1  \mathrm{M} \Omega$ Enclosed in CRS-10A R109 $50  \mathrm{K} \Omega$ Enclosed in CRS-0-1 R110 $50  \mathrm{K} \Omega$ Enclosed in CRSO-1 R111 $50  \mathrm{K} \Omega$ Enclosed in CRSO-1 R112 $40  \mathrm{K} \Omega$ $\frac{1}{2}  \mathrm{Watt}$ $10\%$ Carbon Fixed Resistor R113 $100  \Omega$ $\frac{1}{2}  \mathrm{Watt}$ $10\%$ Carbon Fixed Resistor R114 $1  \mathrm{K} \Omega$ $\frac{1}{2}  \mathrm{Watt}$ $10\%$ Carbon Fixed Resistor R115 $600  \mathrm{K} \Omega$ $\frac{1}{2}  \mathrm{Watt}$ $10\%$ Carbon Fixed Resistor R116 $150  \mathrm{K} \Omega$ $\frac{1}{2}  \mathrm{Watt}$ $10\%$ Carbon Fixed Resistor R117 $1.5  \mathrm{K} \Omega$ $\frac{1}{2}  \mathrm{Watt}$ $10\%$ Carbon Fixed Resistor R118 $15  \mathrm{K} \Omega$ $\frac{1}{2}  \mathrm{Watt}$ $10\%$ Carbon Fixed Resistor R119 $30  \mathrm{K} \Omega$ $\frac{1}{2}  \mathrm{Watt}$ $10\%$ Carbon Fixed Resistor R110 $30  \mathrm{K} \Omega$ $\frac{1}{2}  \mathrm{Watt}$ $10\%$ Carbon Fixed Resistor R111 $30  \mathrm{K} \Omega$ $\frac{1}{2}  \mathrm{Watt}$ $10\%$ Carbon Fixed Resistor R112 $30  \mathrm{K} \Omega$ $\frac{1}{2}  \mathrm{Watt}$ $10\%$ Carbon Fixed Resistor R120 $50  \mathrm{K} \Omega$ $\frac{1}{2}  \mathrm{Watt}$ $10\%$ Carbon Fixed Resistor R121 $30  \mathrm{K} \Omega$ $\frac{1}{2}  \mathrm{Watt}$ $10\%$ Carbon Fixed Resistor R122 $3  \mathrm{K} \Omega$ $\frac{1}{2}  \mathrm{Watt}$ $10\%$ Carbon Fixed Resistor R123 $200  \mathrm{K} \Omega$ $\frac{1}{2}  \mathrm{Watt}$ $10\%$ Carbon Fixed Resistor R124 $200  \mathrm{K} \Omega$ $\frac{1}{2}  \mathrm{Watt}$ $10\%$ Carbon Fixed Resistor R125 $1  \mathrm{K} \Omega$ $\frac{1}{2}  \mathrm{Watt}$ $10\%$ Carbon Fixed Resistor R126 $1  \mathrm{K} \Omega$ $\frac{1}{2}  \mathrm{Watt}$ $10\%$ Carbon Fixed Resistor R127 $6  \mathrm{K} \Omega$ $\frac{1}{2}  \mathrm{Watt}$ $10\%$ Carbon Fixed Resistor R128 $8  \Omega$ $10  \mathrm{Watt}$ $10\%$ Carbon Fixed Resistor R130 $5  \mathrm{K} \Omega$ $\frac{1}{2}  \mathrm{Watt}$ $10\%$ Carbon Fixed Resistor R131 $3  \mathrm{K} \Omega$ $\frac{1}{2}  \mathrm{Watt}$ $10\%$ Carbon Fixed Resistor			1. 5.					
R102 $15  \mathrm{K}\Omega$ Enclosed in CRSO 2 R103 $100  \mathrm{K}\Omega$ Enclosed in CRSO 2 R104 $2  \mathrm{K}\Omega$ $1/4  \mathrm{Watt}$ $10\%  \mathrm{Carbon}$ Fixed Resistor R105 $50  \mathrm{K}\Omega$ $1/2  \mathrm{Watt}$ $10\%  \mathrm{Carbon}$ Fixed Resistor R106 $2  \mathrm{M}\Omega$ Enclosed in CRS-10A R107 $2  \mathrm{M}\Omega$ Enclosed in CRS-10A R108 $1  \mathrm{M}\Omega$ Enclosed in CRS-10A R109 $50  \mathrm{K}\Omega$ Enclosed in CRS-01 R110 $50  \mathrm{K}\Omega$ Enclosed in CRS-0-1 R111 $50  \mathrm{K}\Omega$ Enclosed in CRSO-1 R112 $40  \mathrm{K}\Omega$ $1/2  \mathrm{Watt}$ $10\%  \mathrm{Carbon}$ Fixed Resistor R113 $100  \Omega$ $1/2  \mathrm{Watt}$ $10\%  \mathrm{Carbon}$ Fixed Resistor R114 $1  \mathrm{K}\Omega$ $1/2  \mathrm{Watt}$ $10\%  \mathrm{Carbon}$ Fixed Resistor R115 $600  \mathrm{K}\Omega$ $1/2  \mathrm{Watt}$ $10\%  \mathrm{Carbon}$ Fixed Resistor R116 $150  \mathrm{K}\Omega$ $1/2  \mathrm{Watt}$ $10\%  \mathrm{Carbon}$ Fixed Resistor R117 $1.5  \mathrm{K}\Omega$ $1/2  \mathrm{Watt}$ $10\%  \mathrm{Carbon}$ Fixed Resistor R118 $15  \mathrm{K}\Omega$ $1/2  \mathrm{Watt}$ $10\%  \mathrm{Carbon}$ Fixed Resistor R119 $30  \mathrm{K}\Omega$ $1/2  \mathrm{Watt}$ $10\%  \mathrm{Carbon}$ Fixed Resistor R120 $50  \mathrm{K}\Omega$ $1/2  \mathrm{Watt}$ $10\%  \mathrm{Carbon}$ Fixed Resistor R121 $30  \mathrm{K}\Omega$ $1/2  \mathrm{Watt}$ $10\%  \mathrm{Carbon}$ Fixed Resistor R122 $3  \mathrm{K}\Omega$ $1/2  \mathrm{Watt}$ $10\%  \mathrm{Carbon}$ Fixed Resistor R123 $200  \mathrm{K}\Omega$ $1/2  \mathrm{Watt}$ $10\%  \mathrm{Carbon}$ Fixed Resistor R124 $200  \mathrm{K}\Omega$ $1/2  \mathrm{Watt}$ $10\%  \mathrm{Carbon}$ Fixed Resistor R125 $1  \mathrm{K}\Omega$ $1/2  \mathrm{Watt}$ $10\%  \mathrm{Carbon}$ Fixed Resistor R126 $1  \mathrm{K}\Omega$ $1/2  \mathrm{Watt}$ $10\%  \mathrm{Carbon}$ Fixed Resistor R127 $1  \mathrm{K}\Omega$ $1/2  \mathrm{Watt}$ $10\%  \mathrm{Carbon}$ Fixed Resistor R128 $1  \mathrm{K}\Omega$ $1/2  \mathrm{Watt}$ $10\%  \mathrm{Carbon}$ Fixed Resistor R129 $1  \mathrm{K}\Omega$ $1/2  \mathrm{Watt}$ $10\%  \mathrm{Carbon}$ Fixed Resistor R129 $1  \mathrm{K}\Omega$ $1/2  \mathrm{Watt}$ $10\%  \mathrm{Carbon}$ Fixed Resistor R128 $1  \mathrm{K}\Omega$ $1/2  \mathrm{Watt}$ $10\%  \mathrm{Carbon}$ Fixed Resistor R129 $1  \mathrm{K}\Omega$ $1/2  \mathrm{Watt}$ $10\%  \mathrm{Carbon}$ Fixed Resistor R129 $1  \mathrm{K}\Omega$ $1/2  \mathrm{Watt}$ $10\%  \mathrm{Carbon}$ Fixed Resistor R129 $1  \mathrm{K}\Omega$ $1/2  \mathrm{Watt}$ $10\%  \mathrm{Carbon}$ Fixed Resistor R130 $1  \mathrm{K}\Omega$ $1/2  \mathrm{Watt}$ $10\%  \mathrm{Carbon}$ Fixed Resistor R131 $1  \mathrm{K}\Omega$						ress	VG2121O1	
R103 $100  \mathrm{K}\Omega$ Enclosed in CRSO 2 R104 $2  \mathrm{K}\Omega$ $1/4  \mathrm{Watt}$ $10\%$ Carbon Fixed Resistor R105 $50  \mathrm{K}\Omega$ $1/2  \mathrm{Watt}$ $10\%$ Carbon Fixed Resistor R106 $2  \mathrm{M}\Omega$ Enclosed in CRS-10A R107 $2  \mathrm{M}\Omega$ Enclosed in CRS-10A R108 $1  \mathrm{M}\Omega$ Enclosed in CRS-10A R109 $50  \mathrm{K}\Omega$ Enclosed in CRS-0-1 R110 $50  \mathrm{K}\Omega$ Enclosed in CRSO-1 R111 $50  \mathrm{K}\Omega$ Enclosed in CRSO-1 R112 $40  \mathrm{K}\Omega$ $1/2  \mathrm{Watt}$ $10\%$ Carbon Fixed Resistor R113 $100  \Omega$ $1/2  \mathrm{Watt}$ $10\%$ Carbon Fixed Resistor R114 $1  \mathrm{K}\Omega$ $1/2  \mathrm{Watt}$ $10\%$ Carbon Fixed Resistor R115 $600  \mathrm{K}\Omega$ $1/2  \mathrm{Watt}$ $10\%$ Carbon Fixed Resistor R116 $150  \mathrm{K}\Omega$ $1/2  \mathrm{Watt}$ $10\%$ Carbon Fixed Resistor R117 $1.5  \mathrm{K}\Omega$ $1/2  \mathrm{Watt}$ $10\%$ Carbon Fixed Resistor R119 $30  \mathrm{K}\Omega$ $1/2  \mathrm{Watt}$ $10\%$ Carbon Fixed Resistor R119 $30  \mathrm{K}\Omega$ $1/2  \mathrm{Watt}$ $10\%$ Carbon Fixed Resistor R120 $50  \mathrm{K}\Omega$ $1/2  \mathrm{Watt}$ $10\%$ Carbon Fixed Resistor R121 $30  \mathrm{K}\Omega$ $1/2  \mathrm{Watt}$ $10\%$ Carbon Fixed Resistor R122 $3  \mathrm{K}\Omega$ $1/2  \mathrm{Watt}$ $10\%$ Carbon Fixed Resistor R123 $200  \mathrm{K}\Omega$ $1/2  \mathrm{Watt}$ $10\%$ Carbon Fixed Resistor R124 $200  \mathrm{K}\Omega$ $1/2  \mathrm{Watt}$ $10\%$ Carbon Fixed Resistor R125 $1  \mathrm{K}\Omega$ $1/2  \mathrm{Watt}$ $10\%$ Carbon Fixed Resistor R126 $1  \mathrm{K}\Omega$ $1/2  \mathrm{Watt}$ $10\%$ Carbon Fixed Resistor R127 $1  \mathrm{K}\Omega$ $1/2  \mathrm{Watt}$ $10\%$ Carbon Fixed Resistor R128 $1  \mathrm{K}\Omega$ $1/2  \mathrm{Watt}$ $10\%$ Carbon Fixed Resistor R129 $1  \mathrm{K}\Omega$ $1/2  \mathrm{Watt}$ $10\%$ Carbon Fixed Resistor R128 $1  \mathrm{K}\Omega$ $1/2  \mathrm{Watt}$ $10\%$ Carbon Fixed Resistor R128 $1  \mathrm{K}\Omega$ $1/2  \mathrm{Watt}$ $10\%$ Carbon Fixed Resistor R129 $1  \mathrm{K}\Omega$ $1/2  \mathrm{Watt}$ $10\%$ Carbon Fixed Resistor R129 $1  \mathrm{K}\Omega$ $1/2  \mathrm{Watt}$ $10\%$ Carbon Fixed Resistor R129 $1  \mathrm{K}\Omega$ $1/2  \mathrm{Watt}$ $10\%$ Carbon Fixed Resistor R129 $1  \mathrm{K}\Omega$ $1/2  \mathrm{Watt}$ $10\%$ Carbon Fixed Resistor R130 $1  \mathrm{K}\Omega$ $1/2  \mathrm{Watt}$ $10\%$ Carbon Fixed Resistor R131 $1  \mathrm{K}\Omega$ $1/2  \mathrm{Watt}$ $10\%$ Carbon Fixed Resistor R131 $1  \mathrm{K}\Omega$ $1/2  \mathrm{Watt}$ $10\%$ Carbon Fixed Resistor R								
R104 $2  K\Omega$ $1/4  Watt$ $10\%$ Carbon Fixed Resistor R105 $50  K\Omega$ $1/2  Watt$ $10\%$ Carbon Fixed Resistor R106 $2  M\Omega$ Enclosed in CRS-10A R107 $2  M\Omega$ Enclosed in CRS-10A R108 $1  M\Omega$ Enclosed in CRS-10A R109 $50  K\Omega$ Enclosed in CRSO-1 R110 $50  K\Omega$ Enclosed in CRSO-1 R111 $50  K\Omega$ Enclosed in CRSO-1 R112 $40  K\Omega$ $1/2  Watt$ $10\%$ Carbon Fixed Resistor R113 $100  \Omega$ $1/2  Watt$ $10\%$ Carbon Fixed Resistor R114 $1  K\Omega$ $1/2  Watt$ $10\%$ Carbon Fixed Resistor R115 $600  K\Omega$ $1/2  Watt$ $10\%$ Carbon Fixed Resistor R116 $150  K\Omega$ $1/2  Watt$ $10\%$ Carbon Fixed Resistor R117 $1.5  K\Omega$ $1/2  Watt$ $10\%$ Carbon Fixed Resistor R119 $100  K\Omega$ $1/2  Watt$ $10\%$ Carbon Fixed Resistor R119 $100  K\Omega$ $1/2  Watt$ $10\%$ Carbon Fixed Resistor R119 $100  K\Omega$ $1/2  Watt$ $10\%$ Carbon Fixed Resistor R120 $100  K\Omega$ $1/2  Watt$ $10\%$ Carbon Fixed Resistor R121 $100  K\Omega$ $1/2  Watt$ $10\%$ Carbon Fixed Resistor R122 $100  K\Omega$ $1/2  Watt$ $10\%$ Carbon Fixed Resistor R123 $100  K\Omega$ $1/2  Watt$ $10\%$ Carbon Fixed Resistor R124 $100  K\Omega$ $1/2  Watt$ $10\%$ Carbon Fixed Resistor R125 $100  K\Omega$ $1/2  Watt$ $10\%$ Carbon Fixed Resistor R126 $100  K\Omega$ $1/2  Watt$ $10\%$ Carbon Fixed Resistor R127 $100  K\Omega$ $1/2  Watt$ $10\%$ Carbon Fixed Resistor R128 $100  K\Omega$ $1/2  Watt$ $10\%$ Carbon Fixed Resistor R129 $100  K\Omega$ $1/2  Watt$ $10\%$ Carbon Fixed Resistor R129 $100  K\Omega$ $1/2  Watt$ $10\%$ Carbon Fixed Resistor R129 $100  K\Omega$ $1/2  Watt$ $10\%$ Carbon Fixed Resistor R129 $100  K\Omega$ $1/2  Watt$ $10\%$ Carbon Fixed Resistor R129 $100  K\Omega$ $1/2  Watt$ $10\%$ Carbon Fixed Resistor R129 $100  K\Omega$ $1/2  Watt$ $10\%$ Carbon Fixed Resistor R130 $100  K\Omega$ $1/2  Watt$ $10\%$ Carbon Fixed Resistor R131 $100  K\Omega$ $1/2  Watt$ $10\%$ Carbon Fixed Resistor R131 $100  K\Omega$ $1/2  Watt$ $10\%$ Carbon Fixed Resistor R131 $100  K\Omega$ $1/2  Watt$ $10\%$ Carbon Fixed Resistor R131 $100  K\Omega$ $1/2  Watt$ $10\%$ Carbon Fixed Resistor R131 $100  K\Omega$ $1/2  Watt$ $10\%$ Carbon Fixed Resistor R131 $100  K\Omega$ $1/2  W$								
R105 $50  \mathrm{K}\Omega$ $\frac{1}{2}  \mathrm{Watt}$ $10\%$ Carbon Fixed Resistor R106 $2  \mathrm{M}\Omega$ Enclosed in CRS-10A R107 $2  \mathrm{M}\Omega$ Enclosed in CRS-10A R108 $1  \mathrm{M}\Omega$ Enclosed in CRS-10A R109 $50  \mathrm{K}\Omega$ Enclosed in CRSO-1 R110 $50  \mathrm{K}\Omega$ Enclosed in CRSO-1 R111 $50  \mathrm{K}\Omega$ Enclosed in CRSO-1 R112 $40  \mathrm{K}\Omega$ $\frac{1}{2}  \mathrm{Watt}$ $10\%$ Carbon Fixed Resistor R113 $100  \Omega$ $\frac{1}{2}  \mathrm{Watt}$ $10\%$ Carbon Fixed Resistor R114 $1  \mathrm{K}\Omega$ $\frac{1}{2}  \mathrm{Watt}$ $10\%$ Carbon Fixed Resistor R115 $600  \mathrm{K}\Omega$ $\frac{1}{2}  \mathrm{Watt}$ $10\%$ Carbon Fixed Resistor R116 $150  \mathrm{K}\Omega$ $\frac{1}{2}  \mathrm{Watt}$ $10\%$ Carbon Fixed Resistor R117 $1.5  \mathrm{K}\Omega$ $\frac{1}{2}  \mathrm{Watt}$ $10\%$ Carbon Fixed Resistor R119 $30  \mathrm{K}\Omega$ $\frac{1}{2}  \mathrm{Watt}$ $10\%$ Carbon Fixed Resistor R119 $30  \mathrm{K}\Omega$ $\frac{1}{2}  \mathrm{Watt}$ $10\%$ Carbon Fixed Resistor R120 $50  \mathrm{K}\Omega$ $\frac{1}{2}  \mathrm{Watt}$ $10\%$ Carbon Fixed Resistor R121 $30  \mathrm{K}\Omega$ $\frac{1}{2}  \mathrm{Watt}$ $10\%$ Carbon Fixed Resistor R122 $30  \mathrm{K}\Omega$ $\frac{1}{2}  \mathrm{Watt}$ $10\%$ Carbon Fixed Resistor R123 $200  \mathrm{K}\Omega$ $\frac{1}{4}  \mathrm{Watt}$ $10\%$ Carbon Fixed Resistor R124 $200  \mathrm{K}\Omega$ $\frac{1}{4}  \mathrm{Watt}$ $10\%$ Carbon Fixed Resistor R125 $1  \mathrm{K}\Omega$ $\frac{1}{4}  \mathrm{Watt}$ $10\%$ Carbon Fixed Resistor R126 $1  \mathrm{K}\Omega$ $\frac{1}{4}  \mathrm{Watt}$ $10\%$ Carbon Fixed Resistor R126 $1  \mathrm{K}\Omega$ $\frac{1}{4}  \mathrm{Watt}$ $10\%$ Carbon Fixed Resistor R127 $6  \mathrm{K}\Omega$ $\frac{1}{4}  \mathrm{Watt}$ $10\%$ Carbon Fixed Resistor R128 $8  \Omega$ $10  \mathrm{Watt}$ $10\%$ Carbon Fixed Resistor R129 $500  \Omega$ $1  \mathrm{Watt}$ $10\%$ Carbon Fixed Resistor R129 $500  \Omega$ $1  \mathrm{Watt}$ $10\%$ Carbon Fixed Resistor R130 $5  \mathrm{K}\Omega$ $\frac{1}{4}  \mathrm{Watt}$ $10\%$ Carbon Fixed Resistor R131 $3  \mathrm{K}\Omega$ $\frac{1}{4}  \mathrm{Watt}$ $10\%$ Carbon Fixed Resistor R131 $3  \mathrm{K}\Omega$ $\frac{1}{4}  \mathrm{Watt}$ $10\%$ Carbon Fixed Resistor R131 $3  \mathrm{K}\Omega$ $\frac{1}{4}  \mathrm{Watt}$ $10\%$ Carbon Fixed Resistor R131 $3  \mathrm{K}\Omega$ $\frac{1}{4}  \mathrm{Watt}$ $10\%$ Carbon Fixed Resistor R131 $3  \mathrm{K}\Omega$ $\frac{1}{4}  \mathrm{Watt}$ $10\%$ Carbon Fixed Resistor R131 $3  \mathrm{K}\Omega$ $\frac{1}{4}  \mathrm{Watt}$ $10\%$ Carbon Fixed Resistor R131 $3  K$	i					Fixed	Resistor	
R107 $2 M\Omega$ Enclosed in CRS-10A R108 $1 M\Omega$ Enclosed in CRS-10A R109 $50 K\Omega$ Enclosed in CRSO-1 R110 $50 K\Omega$ Enclosed in CRSO-1 R111 $50 K\Omega$ Enclosed in CRSO-1 R112 $40 K\Omega$ $\frac{1}{2} Watt$ $10\%$ Carbon Fixed Resistor R113 $100 \Omega$ $\frac{1}{4} Watt$ $10\%$ Carbon Fixed Resistor R114 $1 K\Omega$ $\frac{1}{4} Watt$ $10\%$ Carbon Fixed Resistor R115 $600 K\Omega$ $\frac{1}{2} Watt$ $10\%$ Carbon Fixed Resistor R116 $150 K\Omega$ $\frac{1}{2} Watt$ $10\%$ Carbon Fixed Resistor R117 $1.5 K\Omega$ $\frac{1}{4} Watt$ $10\%$ Carbon Fixed Resistor R118 $15 K\Omega$ $\frac{1}{4} Watt$ $10\%$ Carbon Fixed Resistor R119 $30 K\Omega$ $\frac{1}{2} Watt$ $10\%$ Carbon Fixed Resistor R119 $30 K\Omega$ $\frac{1}{2} Watt$ $10\%$ Carbon Fixed Resistor R120 $50 K\Omega$ $\frac{1}{2} Watt$ $10\%$ Carbon Fixed Resistor R121 $30 K\Omega$ $\frac{1}{2} Watt$ $10\%$ Carbon Fixed Resistor R122 $3 K\Omega$ $\frac{1}{4} Watt$ $10\%$ Carbon Fixed Resistor R123 $200 K\Omega$ $\frac{1}{4} Watt$ $10\%$ Carbon Fixed Resistor R124 $200 K\Omega$ $\frac{1}{4} Watt$ $10\%$ Carbon Fixed Resistor R125 $1 K\Omega$ $\frac{1}{4} Watt$ $10\%$ Carbon Fixed Resistor R126 $1 K\Omega$ $\frac{1}{4} Watt$ $10\%$ Carbon Fixed Resistor R127 $6 K\Omega$ $15 Watt$ $10\%$ Carbon Fixed Resistor R128 $8\Omega$ $10 Watt$ $10\%$ Carbon Fixed Resistor R129 $500 \Omega$ $1 Watt$ $10\%$ Carbon Fixed Resistor R129 $500 \Omega$ $1 Watt$ $10\%$ Carbon Fixed Resistor R130 $5 K\Omega$ $\frac{1}{4} Watt$ $10\%$ Carbon Fixed Resistor R131 $3 K\Omega$ $\frac{1}{4} Watt$ $10\%$ Carbon Fixed Resistor R131 $3 K\Omega$ $\frac{1}{4} Watt$ $10\%$ Carbon Fixed Resistor R131 $3 K\Omega$ $\frac{1}{4} Watt$ $10\%$ Carbon Fixed Resistor R131 $3 K\Omega$ $\frac{1}{4} Watt$ $10\%$ Carbon Fixed Resistor R132 $100 K\Omega$ $\frac{1}{4} Watt$ $10\%$ Carbon Fixed Resistor R131 $3 K\Omega$ $\frac{1}{4} Watt$ $10\%$ Carbon Fixed Resistor R132 $100 K\Omega$ $\frac{1}{4} Watt$ $10\%$ Carbon Fixed Resistor R131 $3 K\Omega$ $\frac{1}{4} Watt}$ $10\%$ Carbon Fixed Resistor R131 $3 K\Omega$ $\frac{1}{4} Watt}$ $10\%$ Carbon Fixed Resistor R132 $100 K\Omega$ $\frac{1}{4} Watt}$ $10\%$ Carbon Fixed Resistor R132 $100 K\Omega$ $\frac{1}{4} Watt}$ $10\%$ Carbon Fixed Resistor R131 $100 K\Omega$ $\frac{1}{4} Watt}$ $10\%$ Carbon Fixed Resistor R132 $100 K\Omega$	R105	50 K $\Omega$	½Watt		Carbon	Fixed	Resistor	
R108 $1  M\Omega$ Enclosed in CRS-10A R109 $50  K\Omega$ Enclosed in CRSO-1 R110 $50  K\Omega$ Enclosed in CRSO-1 R111 $50  K\Omega$ Enclosed in CRSO-1 R112 $40  K\Omega$ Enclosed in CRSO-1 R113 $100  \Omega$ ½Watt $10\%$ Carbon Fixed Resistor R113 $100  \Omega$ ½Watt $10\%$ Carbon Fixed Resistor R114 $1  K\Omega$ ½Watt $10\%$ Carbon Fixed Resistor R115 $600  K\Omega$ ½Watt $10\%$ Carbon Fixed Resistor R116 $150  K\Omega$ ½Watt $10\%$ Carbon Fixed Resistor R117 $1.5  K\Omega$ ½Watt $10\%$ Carbon Fixed Resistor R118 $15  K\Omega$ ½Watt $10\%$ Carbon Fixed Resistor R119 $30  K\Omega$ ½Watt $10\%$ Carbon Fixed Resistor R120 $50  K\Omega$ ½Watt $10\%$ Carbon Fixed Resistor R121 $30  K\Omega$ ½Watt $10\%$ Carbon Fixed Resistor R122 $3  K\Omega$ ½Watt $10\%$ Carbon Fixed Resistor R123 $200  K\Omega$ ½Watt $10\%$ Carbon Fixed Resistor R124 $200  K\Omega$ ¼Watt $10\%$ Carbon Fixed Resistor R125 $1  K\Omega$ ¼Watt $10\%$ Carbon Fixed Resistor R126 $1  K\Omega$ ¼Watt $10\%$ Carbon Fixed Resistor R127 $6  K\Omega$ ¼Watt $10\%$ Carbon Fixed Resistor R128 $8  \Omega$ $10\%$ Watt $10\%$ Carbon Fixed Resistor R129 $500  \Omega$ 1 Watt $10\%$ Carbon Fixed Resistor R129 $500  \Omega$ 1 Watt $10\%$ Carbon Fixed Resistor R130 $5  K\Omega$ ¼Watt $10\%$ Carbon Fixed Resistor R131 $3  K\Omega$ ¼Watt $10\%$ Carbon Fixed Resistor R132 $3  K\Omega$ ¼Watt $10\%$ Carbon Fixed Resistor R131 $3  K\Omega$ ¼Watt $10\%$ Carbon Fixed Resistor R132 $3  K\Omega$ ¼Watt $3  K\Omega$ Karbon Fixed Resistor R132 $3  K\Omega$ ¼Watt $3  K\Omega$ Carbon Fixed Resistor R133 $3  K\Omega$ ¼Watt $3  K\Omega$ Carbon Fixed Resistor R133 $3  K\Omega$ ¼Watt $3  K\Omega$ Carbon Fixed Resistor R133 $3  K\Omega$ ¼Watt $3  K\Omega$ Carbon Fixed Resistor R132 $3  K\Omega$ %Watt $3  K\Omega$ Carbon Fixed Resistor R133 $3  K\Omega$ %Watt $3  K\Omega$ Carbon Fixed Resistor R132 $3  K\Omega$ Watt $3  K\Omega$ Carbon Fixed Resistor R133 $3  K\Omega$ Watt $3  K\Omega$ Carbon Fixed Resistor R1	<b>R</b> 106	$2M\Omega$	Enclosed	in	CRS-10A			
R109 $50  \mathrm{K}\Omega$ Enclosed in CRSO-1 R110 $50  \mathrm{K}\Omega$ Enclosed in CRSO-1 R111 $50  \mathrm{K}\Omega$ Enclosed in CRSO-1 R112 $40  \mathrm{K}\Omega$ $\frac{1}{2}  \mathrm{Watt}$ $10\%$ Carbon Fixed Resistor R113 $100  \Omega$ $\frac{1}{4}  \mathrm{Watt}$ $10\%$ Carbon Fixed Resistor R114 $1  \mathrm{K}\Omega$ $\frac{1}{4}  \mathrm{Watt}$ $10\%$ Carbon Fixed Resistor R115 $600  \mathrm{K}\Omega$ $\frac{1}{2}  \mathrm{Watt}$ $10\%$ Carbon Fixed Resistor R116 $150  \mathrm{K}\Omega$ $\frac{1}{2}  \mathrm{Watt}$ $10\%$ Carbon Fixed Resistor R117 $1.5  \mathrm{K}\Omega$ $\frac{1}{4}  \mathrm{Watt}$ $10\%$ Carbon Fixed Resistor R118 $15  \mathrm{K}\Omega$ $\frac{1}{4}  \mathrm{Watt}$ $10\%$ Carbon Fixed Resistor R119 $30  \mathrm{K}\Omega$ $\frac{1}{2}  \mathrm{Watt}$ $10\%$ Carbon Fixed Resistor R120 $50  \mathrm{K}\Omega$ $\frac{1}{2}  \mathrm{Watt}$ $10\%$ Carbon Fixed Resistor R121 $30  \mathrm{K}\Omega$ $\frac{1}{2}  \mathrm{Watt}$ $10\%$ Carbon Fixed Resistor R122 $3  \mathrm{K}\Omega$ $\frac{1}{4}  \mathrm{Watt}$ $10\%$ Carbon Fixed Resistor R123 $200  \mathrm{K}\Omega$ $\frac{1}{4}  \mathrm{Watt}$ $10\%$ Carbon Fixed Resistor R124 $200  \mathrm{K}\Omega$ $\frac{1}{4}  \mathrm{Watt}$ $10\%$ Carbon Fixed Resistor R125 $1  \mathrm{K}\Omega$ $\frac{1}{4}  \mathrm{Watt}$ $10\%$ Carbon Fixed Resistor R126 $1  \mathrm{K}\Omega$ $\frac{1}{4}  \mathrm{Watt}$ $10\%$ Carbon Fixed Resistor R127 $6  \mathrm{K}\Omega$ $\frac{1}{4}  \mathrm{Watt}$ $10\%$ Carbon Fixed Resistor R128 $8  \Omega$ $10  \mathrm{Watt}$ $10\%$ Carbon Fixed Resistor R129 $500  \Omega$ $1  \mathrm{Watt}$ $10\%$ Carbon Fixed Resistor R129 $500  \Omega$ $1  \mathrm{Watt}$ $10\%$ Carbon Fixed Resistor R130 $5  \mathrm{K}\Omega$ $\frac{1}{4}  \mathrm{Watt}$ $10\%$ Carbon Fixed Resistor R131 $3  \mathrm{K}\Omega$ $\frac{1}{4}  \mathrm{Watt}$ $10\%$ Carbon Fixed Resistor R131 $3  \mathrm{K}\Omega$ $\frac{1}{4}  \mathrm{Watt}$ $10\%$ Carbon Fixed Resistor R131 $3  \mathrm{K}\Omega$ $\frac{1}{4}  \mathrm{Watt}$ $10\%$ Carbon Fixed Resistor R131 $3  \mathrm{K}\Omega$ $\frac{1}{4}  \mathrm{Watt}$ $10\%$ Carbon Fixed Resistor R132 $100  \mathrm{K}\Omega$ $\frac{1}{4}  \mathrm{Watt}$ $10\%$ Carbon Fixed Resistor R131 $3  \mathrm{K}\Omega$ $\frac{1}{4}  \mathrm{Watt}$ $10\%$ Carbon Fixed Resistor R132 $100  \mathrm{K}\Omega$ $\frac{1}{4}  \mathrm{Watt}$ $10\%$ Carbon Fixed Resistor R131 $100  \mathrm{K}\Omega$ $\frac{1}{4}  \mathrm{Watt}$ $10\%$ Carbon Fixed Resistor R131 $100  \mathrm{K}\Omega$ $\frac{1}{4}  \mathrm{Watt}$ $10\%$ Carbon Fixed Resistor R131 $100  \mathrm{K}\Omega$	R107	2 M $\Omega$	Enclosed	in	CRS-10A			
R110 $50  \mathrm{K}\Omega$ Enclosed in CRSO-1 R111 $50  \mathrm{K}\Omega$ Enclosed in CRSO-1 R112 $40  \mathrm{K}\Omega$ $\frac{1}{2}  \mathrm{Watt}$ $10\%$ Carbon Fixed Resistor R113 $100  \Omega$ $\frac{1}{4}  \mathrm{Watt}$ $10\%$ Carbon Fixed Resistor R114 $1  \mathrm{K}\Omega$ $\frac{1}{4}  \mathrm{Watt}$ $10\%$ Carbon Fixed Resistor R115 $600  \mathrm{K}\Omega$ $\frac{1}{2}  \mathrm{Watt}$ $10\%$ Carbon Fixed Resistor R116 $150  \mathrm{K}\Omega$ $\frac{1}{2}  \mathrm{Watt}$ $10\%$ Carbon Fixed Resistor R117 $1.5  \mathrm{K}\Omega$ $\frac{1}{4}  \mathrm{Watt}$ $10\%$ Carbon Fixed Resistor R118 $15  \mathrm{K}\Omega$ $\frac{1}{4}  \mathrm{Watt}$ $10\%$ Carbon Fixed Resistor R119 $30  \mathrm{K}\Omega$ $\frac{1}{2}  \mathrm{Watt}$ $10\%$ Carbon Fixed Resistor R120 $50  \mathrm{K}\Omega$ $\frac{1}{2}  \mathrm{Watt}$ $10\%$ Carbon Fixed Resistor R121 $30  \mathrm{K}\Omega$ $\frac{1}{2}  \mathrm{Watt}$ $10\%$ Carbon Fixed Resistor R122 $3  \mathrm{K}\Omega$ $\frac{1}{4}  \mathrm{Watt}$ $10\%$ Carbon Fixed Resistor R123 $200  \mathrm{K}\Omega$ $\frac{1}{4}  \mathrm{Watt}$ $10\%$ Carbon Fixed Resistor R124 $200  \mathrm{K}\Omega$ $\frac{1}{4}  \mathrm{Watt}$ $10\%$ Carbon Fixed Resistor R125 $1  \mathrm{K}\Omega$ $\frac{1}{4}  \mathrm{Watt}$ $10\%$ Carbon Fixed Resistor R126 $1  \mathrm{K}\Omega$ $\frac{1}{4}  \mathrm{Watt}$ $10\%$ Carbon Fixed Resistor R127 $6  \mathrm{K}\Omega$ $\frac{1}{4}  \mathrm{Watt}$ $10\%$ Carbon Fixed Resistor R128 $8  \Omega$ $10  \mathrm{Watt}$ $10\%$ Carbon Fixed Resistor R129 $500  \Omega$ $1  \mathrm{Watt}$ $10\%$ Carbon Fixed Resistor R130 $5  \mathrm{K}\Omega$ $\frac{1}{4}  \mathrm{Watt}$ $10\%$ Carbon Fixed Resistor R131 $3  \mathrm{K}\Omega$ $\frac{1}{4}  \mathrm{Watt}$ $10\%$ Carbon Fixed Resistor R131 $3  \mathrm{K}\Omega$ $\frac{1}{4}  \mathrm{Watt}$ $10\%$ Carbon Fixed Resistor	R108		Enclosed	in	CRS-10A			
R111 $50  \mathrm{K}\Omega$ Enclosed in CRSO-1 R112 $40  \mathrm{K}\Omega$ $1/2  \mathrm{Watt}$ $10\%$ Carbon Fixed Resistor R113 $100  \Omega$ $1/4  \mathrm{Watt}$ $10\%$ Carbon Fixed Resistor R114 $1  \mathrm{K}\Omega$ $1/4  \mathrm{Watt}$ $10\%$ Carbon Fixed Resistor R115 $600  \mathrm{K}\Omega$ $1/2  \mathrm{Watt}$ $10\%$ Carbon Fixed Resistor R116 $150  \mathrm{K}\Omega$ $1/2  \mathrm{Watt}$ $10\%$ Carbon Fixed Resistor R117 $1.5  \mathrm{K}\Omega$ $1/2  \mathrm{Watt}$ $10\%$ Carbon Fixed Resistor R118 $15  \mathrm{K}\Omega$ $1/2  \mathrm{Watt}$ $10\%$ Carbon Fixed Resistor R119 $30  \mathrm{K}\Omega$ $1/2  \mathrm{Watt}$ $10\%$ Carbon Fixed Resistor R120 $50  \mathrm{K}\Omega$ $1/2  \mathrm{Watt}$ $10\%$ Carbon Fixed Resistor R121 $30  \mathrm{K}\Omega$ $1/2  \mathrm{Watt}$ $10\%$ Carbon Fixed Resistor R122 $3  \mathrm{K}\Omega$ $1/2  \mathrm{Watt}$ $10\%$ Carbon Fixed Resistor R123 $200  \mathrm{K}\Omega$ $1/2  \mathrm{Watt}$ $10\%$ Carbon Fixed Resistor R124 $200  \mathrm{K}\Omega$ $1/2  \mathrm{Watt}$ $10\%$ Carbon Fixed Resistor R125 $1  \mathrm{K}\Omega$ $1/2  \mathrm{Watt}$ $10\%$ Carbon Fixed Resistor R126 $1  \mathrm{K}\Omega$ $1/2  \mathrm{Watt}$ $10\%$ Carbon Fixed Resistor R127 $6  \mathrm{K}\Omega$ $1/2  \mathrm{Watt}$ $10\%$ Carbon Fixed Resistor R128 $8  \Omega$ $10  \mathrm{Watt}$ $10\%$ Carbon Fixed Resistor R129 $500  \Omega$ $1  \mathrm{Watt}$ $10\%$ Carbon Fixed Resistor R130 $5  \mathrm{K}\Omega$ $1/2  \mathrm{Watt}$ $10\%$ Carbon Fixed Resistor R131 $3  \mathrm{K}\Omega$ $1/2  \mathrm{Watt}$ $10\%$ Carbon Fixed Resistor R132 $100  \mathrm{K}\Omega$ $1/2  \mathrm{Watt}$ $10\%$ Carbon Fixed Resistor								
Ri12 $40  \mathrm{K}\Omega$ $1/2  \mathrm{Watt}$ $10\%$ Carbon Fixed Resistor Ri13 $100  \Omega$ $1/4  \mathrm{Watt}$ $10\%$ Carbon Fixed Resistor Ri14 $1  \mathrm{K}\Omega$ $1/4  \mathrm{Watt}$ $10\%$ Carbon Fixed Resistor Ri15 $600  \mathrm{K}\Omega$ $1/2  \mathrm{Watt}$ $10\%$ Carbon Fixed Resistor Ri16 $150  \mathrm{K}\Omega$ $1/2  \mathrm{Watt}$ $10\%$ Carbon Fixed Resistor Ri16 $150  \mathrm{K}\Omega$ $1/2  \mathrm{Watt}$ $10\%$ Carbon Fixed Resistor Ri17 $1.5  \mathrm{K}\Omega$ $1/4  \mathrm{Watt}$ $10\%$ Carbon Fixed Resistor Ri18 $15  \mathrm{K}\Omega$ $1/4  \mathrm{Watt}$ $10\%$ Carbon Fixed Resistor Ri19 $30  \mathrm{K}\Omega$ $1/2  \mathrm{Watt}$ $10\%$ Carbon Fixed Resistor Ri20 $50  \mathrm{K}\Omega$ $1/2  \mathrm{Watt}$ $10\%$ Carbon Fixed Resistor Ri21 $30  \mathrm{K}\Omega$ $1/2  \mathrm{Watt}$ $10\%$ Carbon Fixed Resistor Ri22 $3  \mathrm{K}\Omega$ $1/4  \mathrm{Watt}$ $10\%$ Carbon Fixed Resistor Ri23 $200  \mathrm{K}\Omega$ $1/4  \mathrm{Watt}$ $10\%$ Carbon Fixed Resistor Ri24 $200  \mathrm{K}\Omega$ $1/4  \mathrm{Watt}$ $10\%$ Carbon Fixed Resistor Ri25 $1  \mathrm{K}\Omega$ $1/4  \mathrm{Watt}$ $10\%$ Carbon Fixed Resistor Ri26 $1  \mathrm{K}\Omega$ $1/4  \mathrm{Watt}$ $10\%$ Carbon Fixed Resistor Ri27 $6  \mathrm{K}\Omega$ $1/4  \mathrm{Watt}$ $10\%$ Carbon Fixed Resistor Ri28 $8  \Omega$ $10  \mathrm{Watt}$ $10\%$ Carbon Fixed Resistor Ri29 $500  \Omega$ $1  \mathrm{Watt}$ $10\%$ Carbon Fixed Resistor Ri29 $500  \Omega$ $1  \mathrm{Watt}$ $10\%$ Carbon Fixed Resistor Ri30 $5  \mathrm{K}\Omega$ $1/4  \mathrm{Watt}$ $10\%$ Carbon Fixed Resistor Ri31 $3  \mathrm{K}\Omega$ $1/4  \mathrm{Watt}$ $10\%$ Carbon Fixed Resistor Ri31 $3  \mathrm{K}\Omega$ $1/4  \mathrm{Watt}$ $10\%$ Carbon Fixed Resistor Ri31 $3  \mathrm{K}\Omega$ $1/4  \mathrm{Watt}$ $10\%$ Carbon Fixed Resistor Ri31 $3  \mathrm{K}\Omega$ $1/4  \mathrm{Watt}$ $10\%$ Carbon Fixed Resistor Ri32 $100  \mathrm{K}\Omega$								
R113 $100 \Omega$ $\frac{1}{4}$ Watt $10\%$ Carbon Fixed Resistor R114 $1  \mathrm{K}\Omega$ $\frac{1}{4}$ Watt $10\%$ Carbon Fixed Resistor R115 $600  \mathrm{K}\Omega$ $\frac{1}{2}$ Watt $10\%$ Carbon Fixed Resistor R116 $150  \mathrm{K}\Omega$ $\frac{1}{2}$ Watt $10\%$ Carbon Fixed Resistor R117 $1.5  \mathrm{K}\Omega$ $\frac{1}{4}$ Watt $10\%$ Carbon Fixed Resistor R118 $15  \mathrm{K}\Omega$ $\frac{1}{4}$ Watt $10\%$ Carbon Fixed Resistor R119 $30  \mathrm{K}\Omega$ $\frac{1}{2}$ Watt $10\%$ Carbon Fixed Resistor R120 $50  \mathrm{K}\Omega$ $\frac{1}{2}$ Watt $10\%$ Carbon Fixed Resistor R121 $30  \mathrm{K}\Omega$ $\frac{1}{2}$ Watt $10\%$ Carbon Fixed Resistor R122 $3  \mathrm{K}\Omega$ $\frac{1}{4}$ Watt $10\%$ Carbon Fixed Resistor R123 $200  \mathrm{K}\Omega$ $\frac{1}{4}$ Watt $10\%$ Carbon Fixed Resistor R124 $200  \mathrm{K}\Omega$ $\frac{1}{4}$ Watt $10\%$ Carbon Fixed Resistor R125 $1  \mathrm{K}\Omega$ $\frac{1}{4}$ Watt $10\%$ Carbon Fixed Resistor R126 $1  \mathrm{K}\Omega$ $\frac{1}{4}$ Watt $10\%$ Carbon Fixed Resistor R127 $6  \mathrm{K}\Omega$ $\frac{1}{4}$ Watt $10\%$ Carbon Fixed Resistor R128 $8  \Omega$ $10  \mathrm{Watt}$ Wire Wound Resistor R129 $500  \Omega$ $1  \mathrm{Watt}$ $10\%$ Carbon Fixed Resistor R130 $5  \mathrm{K}\Omega$ $\frac{1}{4}$ Watt $10\%$ Carbon Fixed Resistor R131 $3  \mathrm{K}\Omega$ $\frac{1}{4}$ Watt $10\%$ Carbon Fixed Resistor R131 $3  \mathrm{K}\Omega$ $\frac{1}{4}$ Watt $10\%$ Carbon Fixed Resistor R131 $3  \mathrm{K}\Omega$ $\frac{1}{4}$ Watt $10\%$ Carbon Fixed Resistor R132 $8  \mathrm{K}\Omega$ $\frac{1}{4}$ Watt $\frac{1}{4}$ Carbon Fixed Resistor R131 $\frac{1}{4}$ R00 R130 R131 $\frac{1}{4}$ R00 R131 R132 R100 R132 R100 R131 R132 R100 R132 R1331 R132 R100 R132 R1331 R132 R100 R132 R1331 R1331 R134 R134 R135 R135 R135 R135 R135 R135 R135 R135						<b>5.</b> .		
R114								
R115 $600  \mathrm{K}\Omega$ $\frac{1}{2} \mathrm{Watt}$ $10\%$ Carbon Fixed Resistor R116 $150  \mathrm{K}\Omega$ $\frac{1}{2} \mathrm{Watt}$ $10\%$ Carbon Fixed Resistor R117 $1.5  \mathrm{K}\Omega$ $\frac{1}{4} \mathrm{Watt}$ $10\%$ Carbon Fixed Resistor R118 $15  \mathrm{K}\Omega$ $\frac{1}{4} \mathrm{Watt}$ $10\%$ Carbon Fixed Resistor R119 $30  \mathrm{K}\Omega$ $\frac{1}{2} \mathrm{Watt}$ $10\%$ Carbon Fixed Resistor R120 $50  \mathrm{K}\Omega$ $\frac{1}{2} \mathrm{Watt}$ $10\%$ Carbon Fixed Resistor R121 $30  \mathrm{K}\Omega$ $\frac{1}{2} \mathrm{Watt}$ $10\%$ Carbon Fixed Resistor R122 $3  \mathrm{K}\Omega$ $\frac{1}{2} \mathrm{Watt}$ $10\%$ Carbon Fixed Resistor R123 $200  \mathrm{K}\Omega$ $\frac{1}{4} \mathrm{Watt}$ $10\%$ Carbon Fixed Resistor R124 $200  \mathrm{K}\Omega$ $\frac{1}{4} \mathrm{Watt}$ $10\%$ Carbon Fixed Resistor R125 $1  \mathrm{K}\Omega$ $\frac{1}{4} \mathrm{Watt}$ $10\%$ Carbon Fixed Resistor R126 $1  \mathrm{K}\Omega$ $\frac{1}{4} \mathrm{Watt}$ $10\%$ Carbon Fixed Resistor R127 $6  \mathrm{K}\Omega$ $15 \mathrm{Watt}$ $10\%$ Carbon Fixed Resistor R128 $8  \Omega$ $10 \mathrm{Watt}$ $10\%$ Carbon Fixed Resistor R129 $500  \Omega$ $1  \mathrm{Watt}$ $10\%$ Carbon Fixed Resistor R130 $5  \mathrm{K}\Omega$ $\frac{1}{4} \mathrm{Watt}$ $10\%$ Carbon Fixed Resistor R131 $3  \mathrm{K}\Omega$ $\frac{1}{4} \mathrm{Watt}$ $10\%$ Carbon Fixed Resistor R131 $3  \mathrm{K}\Omega$ $\frac{1}{4} \mathrm{Watt}$ $10\%$ Carbon Fixed Resistor R131 $3  \mathrm{K}\Omega$ $\frac{1}{4} \mathrm{Watt}$ $10\%$ Carbon Fixed Resistor R132 $000  \mathrm{K}\Omega$ $\frac{1}{4} \mathrm{Watt}$ $10\%$ Carbon Fixed Resistor R131 $000  \mathrm{K}\Omega$ $\frac{1}{4} \mathrm{Watt}$ $10\%$ Carbon Fixed Resistor R132 $000  \mathrm{K}\Omega$ $\frac{1}{4} \mathrm{Watt}$ $10\%$ Carbon Fixed Resistor R132 $000  \mathrm{K}\Omega$ $\frac{1}{4} \mathrm{Watt}$ $10\%$ Carbon Fixed Resistor R132 $000  \mathrm{K}\Omega$ $\frac{1}{4} \mathrm{Watt}$ $10\%$ Carbon Fixed Resistor R132 $000  \mathrm{K}\Omega$ $\frac{1}{4} \mathrm{Watt}$ $10\%$ Carbon Fixed Resistor R132 $000  \mathrm{K}\Omega$ $\frac{1}{4} \mathrm{Watt}$ $10\%$ Carbon Fixed Resistor R132 $000  \mathrm{K}\Omega$ $\frac{1}{4} \mathrm{Watt}$ $10\%$ Carbon Fixed Resistor R132 $000  \mathrm{K}\Omega$ $\frac{1}{4} \mathrm{Watt}$ $10\%$ Carbon Fixed Resistor R132 $000  \mathrm{K}\Omega$ $\frac{1}{4} \mathrm{Watt}$ $10\%$ Carbon Fixed Resistor R132 $000  \mathrm{K}\Omega$ $\frac{1}{4} \mathrm{Watt}$ $10\%$ Carbon Fixed Resistor R132 $000  \mathrm{K}\Omega$								
R116 $150  \mathrm{K}\Omega$ $1/2  \mathrm{Watt}$ $10\%$ Carbon Fixed Resistor R117 $1.5  \mathrm{K}\Omega$ $1/4  \mathrm{Watt}$ $10\%$ Carbon Fixed Resistor R118 $15  \mathrm{K}\Omega$ $1/4  \mathrm{Watt}$ $10\%$ Carbon Fixed Resistor R119 $30  \mathrm{K}\Omega$ $1/2  \mathrm{Watt}$ $10\%$ Carbon Fixed Resistor R120 $50  \mathrm{K}\Omega$ $1/2  \mathrm{Watt}$ $10\%$ Carbon Fixed Resistor R121 $30  \mathrm{K}\Omega$ $1/2  \mathrm{Watt}$ $10\%$ Carbon Fixed Resistor R122 $3  \mathrm{K}\Omega$ $1/2  \mathrm{Watt}$ $10\%$ Carbon Fixed Resistor R123 $200  \mathrm{K}\Omega$ $1/2  \mathrm{Watt}$ $10\%$ Carbon Fixed Resistor R124 $200  \mathrm{K}\Omega$ $1/2  \mathrm{Watt}$ $10\%$ Carbon Fixed Resistor R125 $1  \mathrm{K}\Omega$ $1/2  \mathrm{Watt}$ $10\%$ Carbon Fixed Resistor R126 $1  \mathrm{K}\Omega$ $1/2  \mathrm{Watt}$ $10\%$ Carbon Fixed Resistor R127 $6  \mathrm{K}\Omega$ $1/2  \mathrm{Watt}$ $10\%$ Carbon Fixed Resistor R128 $8  \Omega$ $10\%$ $10\%$ Carbon Fixed Resistor R129 $500  \Omega$ $1  \mathrm{Watt}$ $10\%$ Carbon Fixed Resistor R130 $5  \mathrm{K}\Omega$ $1/2  \mathrm{Watt}$ $10\%$ Carbon Fixed Resistor R131 $3  \mathrm{K}\Omega$ $1/2  \mathrm{Watt}$ $10\%$ Carbon Fixed Resistor R131 $3  \mathrm{K}\Omega$ $1/2  \mathrm{Watt}$ $10\%$ Carbon Fixed Resistor R131 $3  \mathrm{K}\Omega$ $1/2  \mathrm{Watt}$ $10\%$ Carbon Fixed Resistor R132 $100  \mathrm{K}\Omega$ $1/2  \mathrm{Watt}$ $10\%$ Carbon Fixed Resistor R131 $3  \mathrm{K}\Omega$ $1/2  \mathrm{Watt}$ $10\%$ Carbon Fixed Resistor R132 $100  \mathrm{K}\Omega$ $1/2  \mathrm{Watt}$ $10\%$ Carbon Fixed Resistor R131 $100  \mathrm{K}\Omega$ $1/2  \mathrm{Watt}$ $10\%$ Carbon Fixed Resistor R132 $100  \mathrm{K}\Omega$ $1/2  \mathrm{Watt}$ $10\%$ Carbon Fixed Resistor R132 $100  \mathrm{K}\Omega$ $1/2  \mathrm{Watt}$ $10\%$ Carbon Fixed Resistor R132 $100  \mathrm{K}\Omega$ $1/2  \mathrm{Watt}$ $10\%$ Carbon Fixed Resistor R132 $100  \mathrm{K}\Omega$ $1/2  \mathrm{Watt}$ $10\%$ Carbon Fixed Resistor R132 $100  \mathrm{K}\Omega$								
R117								
$\begin{array}{cccccccccccccccccccccccccccccccccccc$								
R119 $30  \mathrm{K}\Omega$ $10\%$ Carbon Fixed Resistor R120 $50  \mathrm{K}\Omega$ $12\%$ Watt $10\%$ Carbon Fixed Resistor R121 $30  \mathrm{K}\Omega$ $12\%$ Watt $10\%$ Carbon Fixed Resistor R122 $3  \mathrm{K}\Omega$ $14\%$ Watt $10\%$ Carbon Fixed Resistor R123 $200  \mathrm{K}\Omega$ $14\%$ Watt $10\%$ Carbon Fixed Resistor R124 $200  \mathrm{K}\Omega$ $14\%$ Watt $10\%$ Carbon Fixed Resistor R125 $1  \mathrm{K}\Omega$ $14\%$ Watt $10\%$ Carbon Fixed Resistor R126 $1  \mathrm{K}\Omega$ $14\%$ Watt $10\%$ Carbon Fixed Resistor R127 $6  \mathrm{K}\Omega$ $15\%$ Wire Wound Resistor R128 $8  \Omega$ $10\%$ Watt $10\%$ Carbon Fixed Resistor R129 $500  \Omega$ $1  \mathrm{Watt}$ $10\%$ Carbon Fixed Resistor R130 $5  \mathrm{K}\Omega$ $15\%$ Watt $10\%$ Carbon Fixed Resistor R131 $3  \mathrm{K}\Omega$ $15\%$ Watt $10\%$ Carbon Fixed Resistor R131 $3  \mathrm{K}\Omega$ $15\%$ Watt $10\%$ Carbon Fixed Resistor R132 $100  \mathrm{K}\Omega$ $15\%$ Watt $10\%$ Carbon Fixed Resistor R132 $100  \mathrm{K}\Omega$ $15\%$ Watt $10\%$ Carbon Fixed Resistor R132 $100  \mathrm{K}\Omega$ $15\%$								
R120 $50  \mathrm{K}\Omega$ $1/2  \mathrm{Watt}$ $10\%$ Carbon Fixed Resistor R121 $30  \mathrm{K}\Omega$ $1/2  \mathrm{Watt}$ $10\%$ Carbon Fixed Resistor R122 $3  \mathrm{K}\Omega$ $1/4  \mathrm{Watt}$ $10\%$ Carbon Fixed Resistor R123 $200  \mathrm{K}\Omega$ $1/4  \mathrm{Watt}$ $10\%$ Carbon Fixed Resistor R124 $200  \mathrm{K}\Omega$ $1/4  \mathrm{Watt}$ $10\%$ Carbon Fixed Resistor R125 $1  \mathrm{K}\Omega$ $1/4  \mathrm{Watt}$ $10\%$ Carbon Fixed Resistor R126 $1  \mathrm{K}\Omega$ $1/4  \mathrm{Watt}$ $10\%$ Carbon Fixed Resistor R127 $6  \mathrm{K}\Omega$ $1/4  \mathrm{Watt}$ $10\%$ Carbon Fixed Resistor R128 $8  \Omega$ $10  \mathrm{Watt}$ $10\%$ Carbon Fixed Resistor R129 $500  \Omega$ $1  \mathrm{Watt}$ $10\%$ Carbon Fixed Resistor R130 $5  \mathrm{K}\Omega$ $1/4  \mathrm{Watt}$ $10\%$ Carbon Fixed Resistor R131 $3  \mathrm{K}\Omega$ $1/4  \mathrm{Watt}$ $10\%$ Carbon Fixed Resistor R131 $3  \mathrm{K}\Omega$ $1/4  \mathrm{Watt}$ $10\%$ Carbon Fixed Resistor R132 $100  \mathrm{K}\Omega$ $1/4  \mathrm{Watt}$ $10\%$ Carbon Fixed Resistor R132 $100  \mathrm{K}\Omega$ $1/4  \mathrm{Watt}$ $10\%$ Carbon Fixed Resistor R132 $100  \mathrm{K}\Omega$ $1/4  \mathrm{Watt}$ $10\%$ Carbon Fixed Resistor R132 $100  \mathrm{K}\Omega$ $1/4  \mathrm{Watt}$ $10\%$ Carbon Fixed Resistor R132 $100  \mathrm{K}\Omega$ $1/4  \mathrm{Watt}$ $10\%$ Carbon Fixed Resistor R132 $100  \mathrm{K}\Omega$								
R122 $3  \mathrm{K}\Omega$ $1  \mathrm{W}$ $10  \mathrm{W}$ Carbon Fixed Resistor R123 $200  \mathrm{K}\Omega$ $1  \mathrm{W}$ $10  \mathrm{W}$ Carbon Fixed Resistor R124 $200  \mathrm{K}\Omega$ $1  \mathrm{W}$ $10  \mathrm{W}$ Carbon Fixed Resistor R125 $1  \mathrm{K}\Omega$ $1  \mathrm{W}$ $10  \mathrm{W}$ Carbon Fixed Resistor R126 $1  \mathrm{K}\Omega$ $1  \mathrm{W}$ $10  \mathrm{W}$ Carbon Fixed Resistor R127 $1  \mathrm{K}\Omega$ $1  \mathrm{W}$ $10  \mathrm{W}$ Carbon Fixed Resistor R128 $1  \mathrm{W}$ $10  \mathrm{W}$ $10  \mathrm{W}$ Carbon Fixed Resistor R129 $1  \mathrm{W}$ $10  \mathrm$	R120	50 K $\Omega$		10%	Carbon	Fixed	Resistor	
R123 $200  \mathrm{K}\Omega$ $\frac{1}{4}  \mathrm{Watt}$ $10\%$ Carbon Fixed Resistor R124 $200  \mathrm{K}\Omega$ $\frac{1}{4}  \mathrm{Watt}$ $10\%$ Carbon Fixed Resistor R125 $1  \mathrm{K}\Omega$ $\frac{1}{4}  \mathrm{Watt}$ $10\%$ Carbon Fixed Resistor R126 $1  \mathrm{K}\Omega$ $\frac{1}{4}  \mathrm{Watt}$ $10\%$ Carbon Fixed Resistor R127 $6  \mathrm{K}\Omega$ $15  \mathrm{Watt}$ Wire Wound Resistor R128 $8  \Omega$ $10  \mathrm{Watt}$ Wire Wound Resistor R129 $500  \Omega$ $1  \mathrm{Watt}$ $10\%$ Carbon Fixed Resistor R130 $5  \mathrm{K}\Omega$ $\frac{1}{4}  \mathrm{Watt}$ $10\%$ Carbon Fixed Resistor R131 $3  \mathrm{K}\Omega$ $\frac{1}{4}  \mathrm{Watt}$ $10\%$ Carbon Fixed Resistor R132 $100  \mathrm{K}\Omega$ $\frac{1}{4}  \mathrm{Watt}$ $10\%$ Carbon Fixed Resistor R132 $100  \mathrm{K}\Omega$ $\frac{1}{4}  \mathrm{Watt}$ $10\%$ Carbon Fixed Resistor R132 $100  \mathrm{K}\Omega$ $\frac{1}{4}  \mathrm{Watt}$ $10\%$ Carbon Fixed Resistor	R121				Carbon	Fixed	Resistor	
R124 200 K $\Omega$ $1/4$ Watt 10% Carbon Fixed Resistor R125 1 K $\Omega$ $1/4$ Watt 10% Carbon Fixed Resistor R126 1 K $\Omega$ $1/4$ Watt 10% Carbon Fixed Resistor R127 6 K $\Omega$ 15Watt Wire Wound Resistor R128 8 $\Omega$ 10Watt Wire Wound Resistor R129 500 $\Omega$ 1 Watt 10% Carbon Fixed Resistor R130 5 K $\Omega$ $1/4$ Watt 10% Carbon Fixed Resistor R131 3 K $\Omega$ $1/4$ Watt 10% Carbon Fixed Resistor R132 100 K $\Omega$ $1/4$ Watt 10% Carbon Fixed Resistor R132 Resistor								
R125 $1 \ K\Omega$ $1 \ M$ Watt $10 \ M$ Carbon Fixed Resistor R126 $1 \ K\Omega$ $1 \ M$ Watt $10 \ M$ Carbon Fixed Resistor R127 $6 \ K\Omega$ $15 \ M$ Wire Wound Resistor R128 $8 \ \Omega$ $10 \ M$ Wire Wound Resistor R129 $500 \ \Omega$ $1 \ M$ Watt $10 \ M$ Carbon Fixed Resistor R130 $5 \ K\Omega$ $1 \ M$ Watt $10 \ M$ Carbon Fixed Resistor R131 $3 \ K\Omega$ $1 \ M$ Watt $10 \ M$ Carbon Fixed Resistor R132 $100 \ K\Omega$ $1 \ M$ Watt $10 \ M$ Carbon Fixed Resistor R132 $100 \ K\Omega$								
R126 $1  \mathrm{K}\Omega$ $1  \mathrm{M}$ $10  \mathrm{M}$ Carbon Fixed Resistor R127 $6  \mathrm{K}\Omega$ $15  \mathrm{Watt}$ Wire Wound Resistor R128 $8  \Omega$ $10  \mathrm{Watt}$ Wire Wound Resistor R129 $500  \Omega$ $1  \mathrm{Watt}$ $10  \mathrm{M}$ Carbon Fixed Resistor R130 $5  \mathrm{K}\Omega$ $1  \mathrm{Watt}$ $10  \mathrm{M}$ Carbon Fixed Resistor R131 $3  \mathrm{K}\Omega$ $1  \mathrm{Watt}$ $10  \mathrm{M}$ Carbon Fixed Resistor R132 $100  \mathrm{K}\Omega$ $1  \mathrm{Watt}$ $10  \mathrm{M}$ Carbon Fixed Resistor R132 $100  \mathrm{K}\Omega$ $10  \mathrm{M}$ $10  \mathrm{M}$ Carbon Fixed Resistor								
R127 $6~K\Omega$ 15Watt Wire Wound Resistor R128 $8~\Omega$ 10Watt Wire Wound Resistor R129 $500~\Omega$ 1 Watt 10% Carbon Fixed Resistor R130 $5~K\Omega$ 1/4 Watt 10% Carbon Fixed Resistor R131 $3~K\Omega$ 1/4 Watt 10% Carbon Fixed Resistor R132 $100~K\Omega$ 1/4 Watt 10% Carbon Fixed Resistor								
R128 8 $\Omega$ 10Watt Wire Wound Resistor R129 500 $\Omega$ 1 Watt 10% Carbon Fixed Resistor R130 5 K $\Omega$ 1/4 Watt 10% Carbon Fixed Resistor R131 3 K $\Omega$ 1/4 Watt 10% Carbon Fixed Resistor R132 100 K $\Omega$ 1/4 Watt 10% Carbon Fixed Resistor								
R129 500 $\Omega$ 1 Watt 10% Carbon Fixed Resistor R130 5 K $\Omega$ 1/4 Watt 10% Carbon Fixed Resistor R131 3 K $\Omega$ 1/4 Watt 10% Carbon Fixed Resistor R132 100 K $\Omega$ 1/4 Watt 10% Carbon Fixed Resistor								
R130 $5\mathrm{K}\Omega$ $1/4\mathrm{Watt}$ 10% Carbon Fixed Resistor R131 $3\mathrm{K}\Omega$ $1/4\mathrm{Watt}$ 10% Carbon Fixed Resistor R132 $100\mathrm{K}\Omega$ $1/4\mathrm{Watt}$ 10% Carbon Fixed Resistor								
R131 $3\mathrm{K}\Omega$ $/4\mathrm{Watt}$ $10\%$ Carbon Fixed Resistor R132 $100\mathrm{K}\Omega$ $/4\mathrm{Watt}$ $10\%$ Carbon Fixed Resistor								
R132 $100\mathrm{K}\Omega$ $^1\!\!4\mathrm{Watt}$ $10\%$ Carbon Fixed Resistor								
	ŀ							
	1						•	

Part No.		· No	omenclature			
R134	170 ΚΩ	1/4 Watt	10% Noise	Less	Resistor	Ī
R135	15 K $\Omega$	1/4 Watt	10% Noise	Less	Resistor	
R136	300 Ω	1/4 Watt	10% Carbon	Fixed	Resistor	
R137	15 KΩ	1/4 Watt	10% Noise	Less	Resistor Resistor	
R138 R139	70 KΩ 15 KΩ	¼Watt ¼Watt	10% Noise 10% Noise	Less Less	Resistor	
R140	16 KΩ	1/4 Watt	10% Carbon	Fixed	Resistor	
R141	5 K $\Omega$	1/4 Watt	10% Carbon	Fixed	Resistor	
R142	12 KΩ	1/4 Watt	10% Carbon	Fixed	Resistor	
R143	3 KΩ 10 Ω	1/4 Watt 1/4 Watt	10% Noise 10% Carbon	Less Fixed	Resistor Resistor	
R144	10 Δ2 12 KΩ	1/4 Watt	10% Carbon	Less	Resistor	
R146	40 KΩ	1/4 Watt	10% Carbon	Fixed	Resistor	
R147	500 K $\Omega$	1/4 Watt	10% Carbon	Fixed	Resistor	
R148	2 ΚΩ	1/4 Watt	10% Carbon	Fixed	Resistor	
R149	50 KΩ	½Watt	10% Noise	Less	Resistor	
R150 R151	100 KΩ 15 KΩ	Enclosed Enclosed	in CRSO-2 in CRSO-2			
R152	100 KΩ	Enclosed	in CRSO-2			
R153	2 ΚΩ	1/4 Watt	10% Carbon	Fixed	Resistor	
R154	50 K $\Omega$	½Watt	10% Carbon	Fixed	Resistor	
R155	$2 M\Omega$	Enclosed	in CRSO-10A			
R156	1 MΩ 2 MΩ	Enclosed	in CRSO-10A in CRSO-10A			
R157 R158	50 KΩ	Enclosed Enclosed	in CRSO-10A in CRSO-1	•		
R159	50 KΩ	Enclosed	in CRSO-1			
R160	50 K $\Omega$	Enclosed	in CRSO-1			
R161	100 $\Omega$	1/4 Watt	10% Carbon	Fixed	Resistor	
R162	1 ΚΩ	1/4 Watt	10% Carbon	Fixed	Resistor	
R163	1.5 KΩ 600 KΩ	⅓Watt ½Watt	10% Carbon 10% Carbon	Fixed Fixed	Resistor Resistor	
R164 R165	150 KΩ	½Watt	10% Carbon	Fixed	Resistor	
<b>R</b> 166	15 KΩ	1/4 Watt	10% Carbon	Fixed	Resistor	
<b>R</b> 167	30 K $\Omega$	½Watt	10% Carbon	Fixed	Resistor	
R168	3 KΩ	1/4 Watt	10% Carbon	Fixed	Resistor	
R169 R170	30 KΩ 200 KΩ	½Watt ¼Watt	10% Carbon 10% Carbon	Fixed Fixed	Resistor Resistor	
R170	200 KΩ	1/4 Watt	10% Carbon	Fixed	Resistor	
R172	1 ΚΩ	1/4 Watt	10% Carbon	Fixed	Resistor	•
R173	1 ΚΩ	1/4 Watt	10% Carbon	Fixed	Resistor	
R174	3 KΩ	1/4 Watt	10% Carbon	Fixed	Resistor	
R175 R176	$\Omega$ 8 $\Omega$	10Watt 1 Watt	Wire Wo	ound Fixed	Resistor Resistor	
R177	1 Ω	2 Watt	-	ound	Resistor	
<b>R</b> 178	зкΩ	1/4 Watt	10% Carbon	Fixed	Resistor	
R179	$\Omega$ 000	15Watt	Wire W	ound	Resistor	
R180	15 KΩ	1/4 Watt	10% Carbon	Fixed	Resistor	
R181	6 KΩ 2 KΩ	30Watt	Wire Wo	ound Fixed	Resistor Resistor	
R182 R183	10 KΩ	⅓ warr ½Watt	10% Carbon	Fixed	Resistor	
R184	100 KΩ	1 Watt	10% Carbon	Fixed	Resistor	
<b>R</b> 185	3.9 K $\Omega$	¼Watt	10% Carbon	Fixed	Resistor	
R186	10 KΩ	1/4 Watt	10% Carbon	Fixed	Resistor	
R187	10 ΚΩ	1/4 Watt	10% Carbon	Fixed	Resistor Resistor	
R188 R189	3.3 KΩ 22 KΩ	2 Watt ¼Watt	10% Carbon 10% Carbon	Fixed Fixed	Resistor	
		, -				
C1	10 pF	250 WV		Ceramic Ceramic	tubular tubular	
C2	50 pF	250 WV	1.100	Ceramic Ceramic	tubular	
C3	0.002 μF	250 WV				
C4	0.001 $\mu$ F	250 WV	- 0-	Ceramic	tubular	
C5	0.001 $\mu$ F	250 W V	<sup>+100</sup> <sub>-0</sub> %	Ceramic	tubular	
C6	10 pF	250 WV	10%	Ceramic	tubular	
C7	0.001 $\mu$ F	250 WV	+100 %	Ceramic	tubular	
L				·		_

Part No.		No	omenclatur	e	
C8	2 pF	250 WV	±0.5 pF	Ceramic	tubular
C9	10 pF	250 WV	±0.5 pF	Ceramic	tubular
C10	20 $\mu$ F	350 WV	electrolytic	Lug termi	nal
C11	0.01 $\mu$ F	250 WV	+100 % - 0%	Ceramic	tubular
C12	$0.002~\mu\mathrm{F}$	250 WV	+100%	Ceramic	tubular
C13	0.01 μF	250 WV	+100%	Ceramic	tubular
C14	0.01 μF	250 WV	+100%	Ceramic	tubular
C15	0.01 μF	250 WV	±100%	Ceramic	tubular
C16	0.01 μF	250 WV	+100%	Ceramic	tubular
C17	0.01 μF	250 WV	+100%	Ceramic	tubular
C18	100 pF	250 WV	- 0/9 10%	Ceramic	tubular
C19	50 pF	250 WV	10%	Ceramic	tubular
C20	50 pF	250 WV	10%	Ceramic	tubular
C21	0.01 $\mu$ F	250 WV	+100%	Ceramic	tubular
C22	40 pF	250 WV	10%	Ceramic	tubular
C23	0.01 $\mu$ F	250 WV	+100%	Ceramic	tubular
C24	0.01 $\mu$ F	250 WV	<sup>+100</sup> / <sub>-0</sub> %	Ceramic	tubular
C25	50 pF	250 WV	10%	Ceramic	tubular
C26	50 pF	250 WV	10%	Ceramic	tubular
C27	100 pF	250 W V	10%	Ceramic	tubular
C28	0.02 $\mu$ F	250 W V	+100%	Ceramic	tubular
C29	0.01 $\mu$ F	250 W V	<sup>+100</sup> %	Ceramic	tubular
C30	100 pF	250 WV	10%	Ceramic	tubular
C31	400 pF	500 WV	10%	Mica	tubular tubular
C32	50 pF	250 WV	10%	Ceramic	
C33	0.01 μF	250 WV	+100%	Ceramic	tubular
C34	$0.05~\mu F$	50 WV	+100%	Ceramic	tubular
C35	0.01 $\mu$ F	250 WV	+100%	Ceramic	tubular
C36	20 pF	250 WV	10%	Ceramic	tubular
C37	100 pF	250 WV	10%	Ceramic Ceramic	tubular tubular
C38 C39	3 pF 0.01 μF	250 WV 400 WV	±0.05 pF 10%	Oil	tubular
C40	0.002 μF	250 WV	+100%	Ceramic	tubular
C41	0.001 μF	250 WV	+100%	Ceramic	tubular
C41	0.001 μF	400 WV	- 0/0 10%	Oil	tubular
C42	0.01 μF	400 WV	10%	Oil	tubular
C44	800 pF	400 WV	10%	Oil	tubular
C45	$0.02~\mu$ F	250 WV	+100%	Ceramic	tubular
C46	0.03 $\mu$ F	50 WV	+100%	Ceramic	tubular
C47	150 pF	250 WV	10%	Ceramic	tubular
C48	100 pF	250 WV	10%	Ceramic	tubular
C49	2000 pF	250 WV	5%	Mica	tubular
C50	1500 pF	250 WV	5%	Mica	tubular
C51	10 μF	12 WV		electrolytic	tubular
C52	ΙμΕ	150 WV 400 WV	10%	electrolytic Oil	tubular tubular
C53 C54	0.001 μF 5 μF	25 WV	10%	electrolytic	tubular
C55	0.01 μF	250 WV	5%	Mica	tubular
C56	3000 pF	250 WV	5%	Mica	tubular
C57	100 pF	250 WV	10%	Ceramic	tubular
C58	100 pF	250 WV	10%	Ceramic	tubular
C59	100 pF	250 WV	10%	Ceramic	tubular
C60	100 pF	250 WV	10%	Ceramic	tubular tubular
C61	100 pF	250 W.V	10% +100%	Ceramic	tubular
C62	0.003 μF	250 WV	+100% - 0%	Ceramic	*
C63	100 pF	250 WV	10%	Ceramic	tubular

# PARTS LIST


Part No.		7	omenclature
C64	0.003 μF	250 WV	+100 % Ceramic tubular
C65	20 μF	350 WV	electrolytic Lug terminal
C66	0.01 $\mu$ F	400 W V	10% Oil tubular
C67	0.01 $\mu$ F	400 W V	10% Oil tubular
C68	82 pF	250 W V	5% Mica tubular
C69	510 pF	250 WV	5% Mica tubular
C70	430 pF	250 WV	5% Mica tubular
C71	82 pF	250 WV	5% Mica tubular
C72	20 μF	180 WV	electrolytic tubular
C73	510 pF	250 WV	5% Mica tubular 5% Mica tubular
C74 C75	430 pF 30 μF	250 WV 10 WV	5% Mica tubular electrolytic tubular
C76	450 pF	500 WV	10% Mica tubular
C75	450 pF	500 WV	10% Mica tubular
C78	0.01 μF	250 WV	10% Ceramic tubular
C79	20 μF	25 WV	10% electrolytic tubular
C80	0.006 μF	250 WV	10% mylar tubular
C81	$0.025~\mu$ F	50 WV	10% mylar tubular
C82	0.01 μF	50 W V	10% mylar tubular
C83	30 $\mu$ F	10 WV	electrolytic tubular
C84	30 $\mu$ F	12 W V	electrolytic tubular
C85	30 $\mu$ F	10 WV	electrolytic tubular
C86	10 $\mu$ F	12 WV	electrolytic tubular
C87	0.05 $\mu$ F	50 W V	10% mylar tubular
C88	100 pF	500 WV	10% Mica tubular
C89	0.01 μF	50 WV	10% mylar tubular
C90	$0.05~\mu$ F	50 WV	10% mylar tubular
C91	30 μF	6 WV	electrolytic tubular 10% Oil tubular
C92 C93	0.02 μF 150 pF	400 WV enclosed	10% Oil tubular in CRSO-2
C93	0.001 μF	400 WV	10% Oil tubular
C95	20 pF	250 WV	10% Ceramic subular
C96	$0.003~\mu F$	enclosed	in CRSO-2
C97	0.03 μF	enclosed	in CRSQ-2
C98	20 μF	350 WV	electrolytic Lug terminal
C99	$0.03~\mu F$	400 WV	10% Oil tubular
C100	$\cdot$ 0.01 $\mu$ F	Enclosed	in CRS-10A
C101	0.005 $\mu$ F	Enclosed	in CRS-10A
C102	0.005 $\mu$ F	Enclosed	in CRS-10A
C103	300 pF	Enclosed	in CRSO-1
C104	200 pF	Enclosed	in CRSO-1
C105	200 pF	Enclosed	in CRSO-1
C106	0.2 μF	250 WV 6 W	M. P condenser
C107 C108	30 μF 20 μF	350 WV	Velectrolytic tubular electrolytic Lug terminal
C106	20 μ1 30 pF	500 WV	electrolytic Lug terminal 10% Mica tubular
C109	0.5 μF	250 WV	10% M. P condenser
C111	0.3 μF	250 WV	10% M. P condenser
C112	$0.3~\mu F$	250 WV	10% M. P condenser
C113	20 μF	500 WV	electrolytic Lug terminal
C114	30 $\mu$ F	10 WV	electrolytic tubular
C115	30 $\mu$ F	12 WV	electrolytic tubular
C116	30 $\mu$ F	10 W V	electrolytic tubular
C117	0.01 $\mu$ F	50 WV	10% mylar tubular
C118	$0.025~\mu$ F	50 W V	10% mylar tubular
C119	$0.006~\mu$ F	50 WV	10% mylar tubular
C120	30 μF	10 WV	electrolytic tubular
C121	10 μF	12 WV	electrolytic tubular
C122	0.05 μF	50 WV	10% mylar tubular 10% Mica tubular
C123	100 pF	500 WV 50 WV	10% Mica tubular 10% mylar tubular
C124	$0.01~\mu  extsf{F}$ $0.05~\mu  extsf{F}$	50 WV	10% mylar tubular
C125 C126	0.05 μr 30 μF	6 W V	electrolytic tubular
C126	0.001 μF	400 WV	10% Oil tubular
C128	150 pF	enclosed	in CRSO-2
	· - * F ·		

Part No.		Ν	omenclature			
C129	0.02 μF	400 WV	10%	Oil	tubular	
C130	20 pF	250 WV	10%	Ceramic	tubular	
C131	0.03 $\mu$ F	Enclosed	in CRSO-2			
C132	0.003 μF	Enclosed	in CRSO-2			
C133	0.01 μF	Enclosed	in CRS-10A			
C134	0.03 μF	400 WV	10%	Oil	tubulat	
C135 C136	0.005 μF 0.005 μF	Enclosed Enclosed	in CRS-10A in CRS-10A			
C137	300 pF	Enclosed	in CRSO-1	•		
C138	200 pF	Enclosed	in CRSO-1			
C139	200 pF	Enclosed	in CRSO-1			
C140	30 $\mu$ F	6 WV	ele	ectrolytic	tubular	
C141	0.2 $\mu$ F	250 WV	10% M. P	condenser		
C142	30 pF	500 WV	10%	Mica	tubular	
C143	0.5 μF	250 WV	10% M. P	condenser		
C144 C145	0.3 μF	250 WV 250 WV	10% M. P 10% M. P	condenser condenser		
C145	0.3 $\mu$ F 0.002 $\mu$ F	250 WV	10% M. F	Ceramic	tubular	
C148	0.002 $\mu$ F	250 WV	10%	Ceramic	tubular	1
C148	0.002 μF	250 WV	10%	Ceramic	tubular	
C144	0.005 μF	500 WV	10%	Ceramic	tubular	
C150	50 μF	50 W V	ele	ectrolytic	tubular	
C151	0.005 $\mu$ F	600 WV	10%	Oil	tubular	1
C152	$0.005~\mu F$	600 WV	10%	Oil	tubular	- 1
C153	200 μF	25 WV		ectrolytic	tubular	i
C154	200 μF	300 WV	electrolytic	Lug termi		l
C155 C156	$200~\mu$ F $20~\mu$ F	300 WV 500 WV	electrolytic electrolytic	Lug termi		- 1
C156	20 μF	25 WV	.,	ectrolytic	tubular	
C158	25 μF	50 WV		ectrolytic	tubular	
C159	200 μF	25 W V		ectrolytic	tubular	
C160	20 μF	500 WV	electrolytic	Lug tetmi	nal	
C161	0.05 $\mu$ F	50 WV	±100%	Ceramic	tubular	1
C162	5 μF	25 WV		ectrolytic	tubular	
C163	0.01 μF	250 WV	10%	Ceramic	tubular	
C164	0.01 $\mu$ F	250 WV	10%	Ceramic	tubular	•
C165	20 $\mu$ F	350 WV	electrolytic	Lug termi		[
C166	100 pF	250 WV	10%	Ceramic	tubular	- 1
C167	$0.002~\mu extsf{F}$	250 WV	10%	Ceramic	tubular	ĺ
VR-1	5 K	$\Omega$ (B) V	ariable Resis	tor Drive	type	
VR-2		_ 1 /	ariable Resis		, ,	
VR-3		. ,	ariable Resis			
VR-4	500 K		ariadle Resis ariable Resis			
VR-5			tup 120 K $\Omega$		type	1
VR-7, VR-			riable Resisto		tion type	
		one contro		·		
VR-9			Variable Resi	stor 24 $\phi$ t	ype	
1/0	,	alance co	•			l
VR-10, VR		$\Omega$ HUM $\Omega$	ariable Resis	tor Driver	type	l
VR-11, VR	-12 100 1	1 1 1 1 1 1 1 1 1 1	parancer			1
VC-1		18 pF Vo		citor		
	-	M. RF T				
VC-2		18 pF Va M. RF T		citor		
VC-3	,	M. KF 1 18 pF Va	/	itor		1
, 5-5		M. oscille				
VC-4			riable Capa	citor		
	(A	M. RF	Tuning)			
VC–5		128 pF Va		citor		
VC :		M. RF 1		·ito-		
VC-6		28 pF Va .M. oscill		пог		
L	(A	uvi. OSCIII	uiVI,			

	Part No.	Nomenclature
	TC-1 TC-2 TC-3 TC-4 TC-5 TC-6	15 pF trimer condenser 15 pF trimer condenser 10 pF trimer condenser 15 pF trimer condenser 15 pF trimer condenser 15 pF trimer condenser
	V1 V2 V3 V4 V5 V6 V7 V8 V9 V10 V11 V12 V13 V14 V15 V16 V17 V18 V19 V20	6CW4 FM. RF. Amp 6CW4 FM. RF. Amp 6AQ8 (ECC 85) FM. oscillator & Mixer 6BA6 (EF 93) FM. 1 st. IF. Amp 6BA6 (EF 94) AM. FM. 2 nd IF. Amp 6AU6 (EF 94) 1 st Limitor 6BA6 (EF 94) AM. RF. Amp 6BA6 (EF 94) AM. RF. Amp 6BA6 (EF 94) AM. RF. Amp 6BA6 (ECC 85) Muting Amp 6AQ8 (ECC 85) MPX. Amp & Indicator Amp 12AU7 (ECC 82) Dual, out & deemphasis 12AX7 (ECC 83) Pre Amp 6AN8, Audio, Amp, Phase, splitter 7591 Power Amp 12AX7 (ECC 83) Pre Amp 6AN8, Audio, Amp, Phase, splitte 7591 Power Amp 12AX7 (ECC 83) Pre Amp 6AN8, Audio, Amp, Phase, splitte 7591 Power Amp 12AX7 (ECC 83) Pre Amp 6AN8, Audio, Amp, Phase, splitte
The state of the s	V21	7591 Power Amp
	TR1~4	transistor 2SB-381  FM. Antenna coil AFC-1
A STATE OF THE PARTY OF THE PAR	L1 L2 L3 L4 ,L5 L6 L7 L8 L9 L10 L11 L12 L13 L14 L15 L16 L17 L18 L19 L20	FM. RF coil 1 µH FM. RF coil 1 µH FM. RF coil 1 µH FM. RF coil 3.5 µH FM. Tuning coil FM. oscillator coil MW. Loop stick Antenna coil MW. RF. coil MW. oscillator coil MPX. coil MFC-5A MPX. coil MFC-5B MPX. coil MFT-4A MPX. coil MPT-4B Filter coil 1 µH Filter coil 1 µH Filter Coil 1 µH Heater Cralk coil
	T1 T2 T3 T4 T5 T6 T7 T3	1 st FM. I.F.I. 10.7 Mc/s 2 nd FM. I.F.T. 10.7 Mc/s 3 rd FM. I.F.T. 10.7 Mc/s 4 th FM. I.F.T. 10.7 Mc/s FM Discriminator transformer 1 st AM. I.F.T. 455 Kc/s 2 nd AM. I.F.T. 455 K/cs output transformer (Primary 6 K $\Omega$ ) (Secondary 8 $\Omega$ , 16 $\Omega$ ) output transformer
	<del>-</del> . <u>:</u>	(Primary 6 K $\Omega$ ) (Secondary 8 $\Omega$ , 16 $\Omega$ ) Power transformer

	Nomenclature
Part No.	
SD-1B	Si, diode. AC (RMS) 180V, ID 500 mA $-65^{\circ}\text{C}{\sim}100^{\circ}\text{C}$
OA-91	Ge, diode, $V_D = 90V I_D = 50 \text{ mA}$ $-55^{\circ}\text{C} \sim 75^{\circ}\text{C}$
MA-301	Variable capacitor (FM. AFC)
TC. O-2P	Selenium diode AC 45V ID 25 mA
JAC-1 JAC-2	Headphone Jack DIN Jack (tape recorder connector)
PU-1 PU-2	input trans connector Power Adjustment for 100V/117V/220V/240V
NL	PL-21A Neon Lamp
PL	Pilot Lamp 6.3V 0.15A Fuse type 6.3V 0.3A
F	Fuse 4A
М	Tuning Indicator
S1(α∼g) S2(α∼g) S2(α∼c)	Input Selector Y-4-8-6 Band Selector Y-3-6-4 Mode Selector Y-3-4-5
SS1 SS2 SS3a, 3b SS4a, 4b SS5a, 5b SS6a, 6b SS7a, 7b SS8a, 8b SS9a, 9b SS10	FM. AFC Switch Mutting Switch Tape Monitor Switch Loudness Switch Low Filter Switch High Filter Switch Presence Switch Speaker Switch Impedance Switch Phase Switch
PS-1	Power Switch
CO-ī, 2	AC, Receptacles

# PARTS LEYOUT

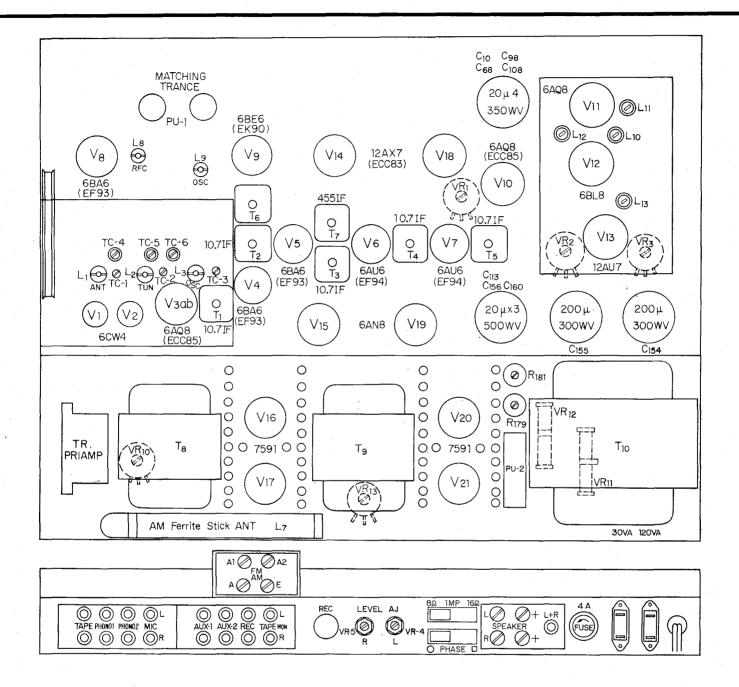

Rı

Rı

RII RII RII RII RII RII

> Ri Ri

> Ra Ra Ra

> RI Ri

> Ri Ri

Ru

R14

R1

Ria Ria Ria

Rъ

R is

R M

R

RI

RI

RI RI RI RI


RI RI

RN RN RN


R N R N R N

O O O


a

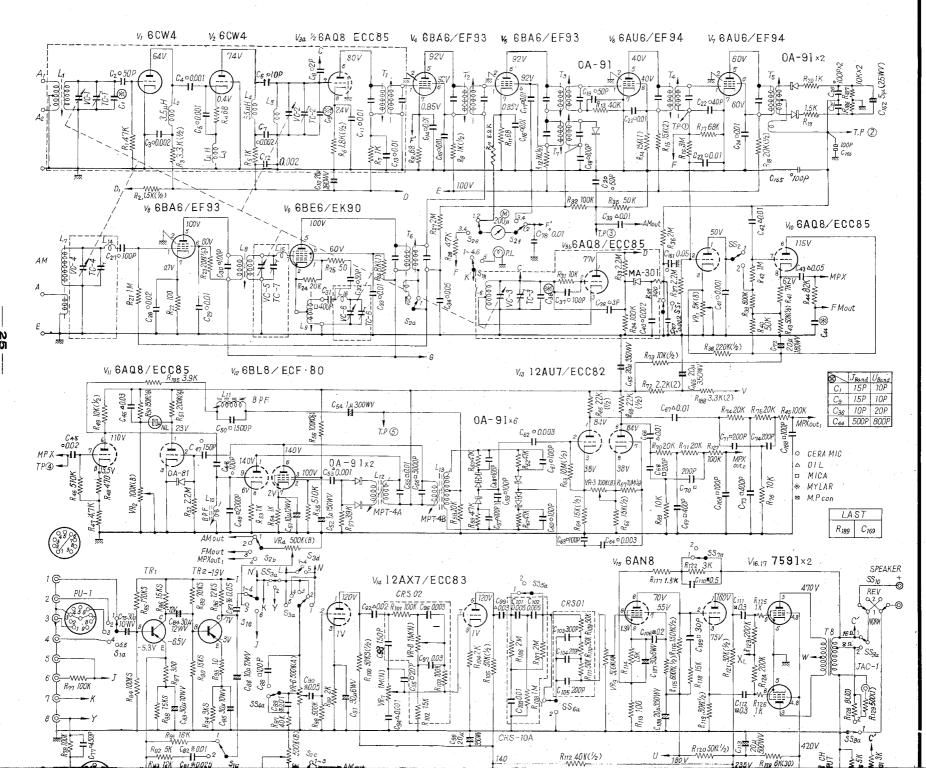




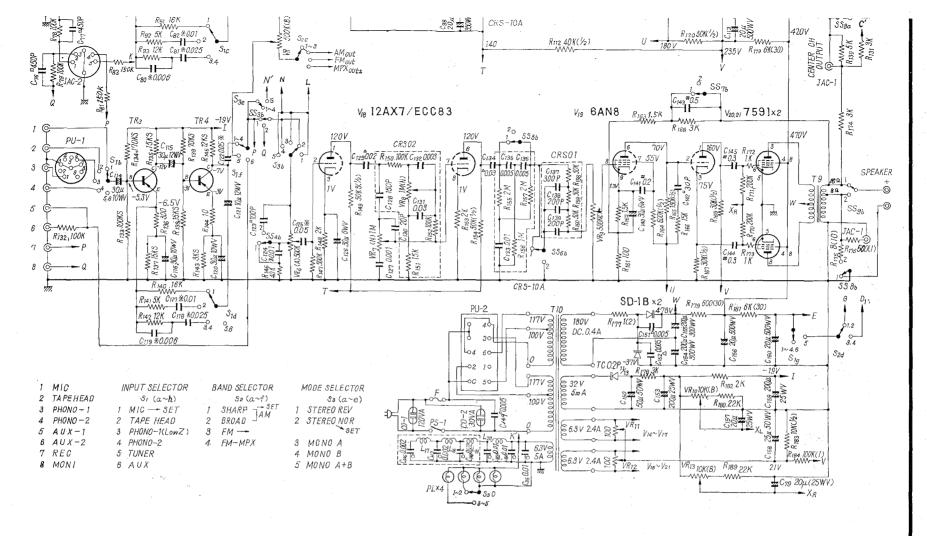

### DISASSEMBLE REMOVALS

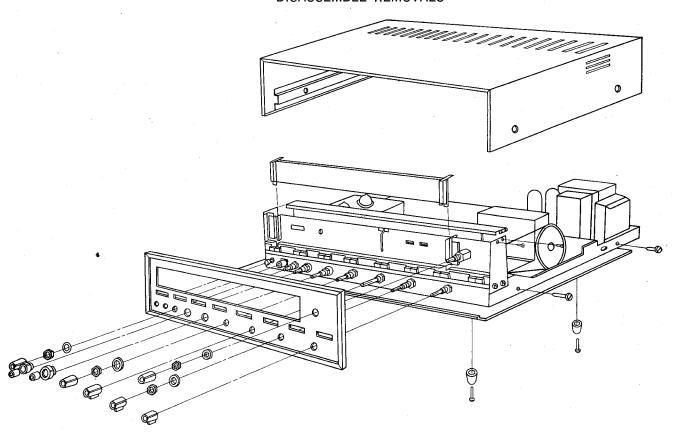

### DIAL CORD STRINGS

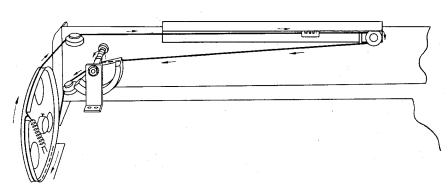

# Sansui

### SANSUI ELECTRIC COMPANY LIMITED

Head Office; 460, Izumi-cho, Suginami-ku, Tokyo, Japan. TEL. 328-0111

Printed in Japan (36050M5)